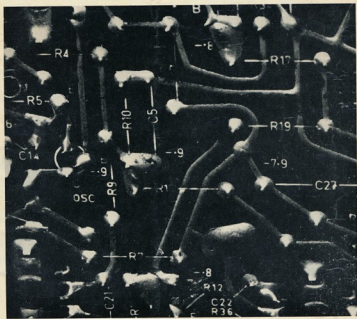


AMATEUR RADIO

JANUARY 1964



Vol. 32, No. 1



2/-

TECH MULTIMETER



300 μ A. movement.
AC and DC voltages:
0-10, 0-50, 0-250, 0-500,
0-1000V.
Current ranges (mA.)
0-1, 0-100, 0-500 mA.
Ohms range: 0-100,000
ohms.
Size: $3\frac{1}{4}$ x $2\frac{1}{2}$ x $1\frac{1}{4}$
inches.
Complete with leads.

Price only 57/6, post paid.

SAKURA CIRCUIT TESTER

Model TR65

Sensitivity: d.c. 20,000 ohms/volt, a.c. 10,000
ohms/volt. Ranges, d.c. volts: 5, 30, 120, 600,
1,200; a.c. volts: 5, 30, 120, 600, 1,200. D.c.
current, 60 μ A., 6 mA., 60 mA., 600 mA. Re-
sistance: 10K, 100K, 1M, 10M ohms. Capacitance
0.001-0.2 μ F., 0.0001-0.01 μ F. Inductance: 30-
3,000H. Decibels: minus 20 to plus 17 db. (9
db. -0.775v. -600 ohms). Dimensions: $4\frac{1}{4}$ x $6\frac{1}{4}$
x $2\frac{1}{2}$ in. Weight 1.3 lbs.

Price £9/10/- inc. tax

AMERICAN POTENTIOMETERS

American Bradley, 2" long, $\frac{1}{4}$ " shaft,
1" diam. Available in following sizes:
10,000, 20,000, 25,000, 30,000, 50,000,
100,000 ohms. Price 2/6 each.

CO-AXIAL CABLE

50 ohm, UR67, 3/8" diam., in 25 yd.
Rolls 30/-; or 1/6 yard.
71 ohm UR32, 3/16" diam., in 100 yard
Rolls £7/10/0.
72 ohm UR70, 3/16" diam., in 27 yd.
Rolls 30/-; or 1/6 yard.
72 ohm, 3/8" 2/- yd., £8/15/0 100 yds.
100 ohm, 3/8" 2/- yd., £8/15/0 100 yds.

ER22 GERMANIUM POCKET RADIO

Complete with earphones and instruc-
tions, 22/6. Aerial wire to suit, 4d. yd.
Ideal Xmas Gift.

LSG11 SIGNAL GENERATOR

120 Kc.-390 Mc.
Freq. range (six
bands): 120 Kc. to
130 Mc. on funda-
mentals; 120 to 390
Mc. on harmonics.
Mod. freq. 400 and
1,000 c.p.s. Tubes:
12BH6, 6AR5. Rec-
tifier: half wave
selenium. Provision
for crystal os-
cillator (not
supplied), 1 to 15
Mc. 100, 117 or
230v. a.c. input, 50-60 c.p.s. Size: $7\frac{1}{2}$ x $10\frac{1}{2}$ x
 $4\frac{1}{2}$ in. Weight: 6 lb.
Price: LSG11, £16/10/6 inc. tax.



Call Books ... 6/- each + 1/- postage

NEW TRANSISTORS IN STOCK

OC45	14/-	OC170	17/6
OC71	10/-	OC171	17/6
OC74	11/-	OC45	14/-

ALUMINIUM CHASSIS

5 x 3 x 2 inch	6/3
6 x 4 x 2 inch	7/-
8 x 5 x 2 inch	10/6
10 x 6 x 2 inch	12/9
13 x 7 x 2 inch	12/9

Also Large Stock of Matrix Boards
and Accessories.

WELL KNOWN MAKE OF RECORDING TAPE

Brand New, in Cartons

Acetate Base, 900 ft. on 5 in. reel	19/6
Acetate Base, 1200 ft. on 7 in. reel	32/6
Polyester Base, 1200 ft. on $5\frac{1}{2}$ in. reel	40/-
Acetate Base, 1800 ft. on 7 in. reel	45/-
Mylar Base, 2400 ft. on 7 in. reel	57/6

METERS

MR1P 0-1 mA., clear plastic case, $1\frac{1}{2}$ " square face, 1" hole	32/6
MR2P 0-1 mA., clear plastic case, $1\frac{1}{2}$ " square face, 1" hole	35/-
P22 0-1 mA., clear plastic case, 2" square face, $1\frac{1}{2}$ " hole	37/6
VR2P Vumeter, -20 +3 db., $1\frac{1}{2}$ " square face, clear face, $1\frac{1}{2}$ " hole	45/-
SR2P Signal Meter, calibrated 9/30 db., clear plastic, few only	40/-
VR3P Vumeter, -20 +3 db., clear plastic, 3" x $3\frac{1}{2}$ "	£3/17/6
VR65 Vumeter, -20 +3 db., black bke- lite case, 3" square	£4/2/6
MO65 0-1 mA., $3\frac{1}{4}$ " round, black bke- lite case	35/-
MO65 0-5 mA., $3\frac{1}{4}$ " round, black bke- lite case	35/-
MO65 0-10 mA., $3\frac{1}{4}$ " round, black bke- lite case	35/-
MO65 0-1 Amp., AC/DC, $3\frac{1}{4}$ " round, black bakelite case	35/-
MO65 0-3 Amp., AC/DC, $3\frac{1}{4}$ " round, black bakelite case	35/-
MO65 0-30 Amp. AC, $3\frac{1}{4}$ " round, black bakelite case	35/-
MO65 0-30 Volts DC, $3\frac{1}{4}$ " round, black bakelite case	35/-
MR2P 0-500 μ A., $1\frac{1}{2}$ " square, clear plastic	37/6
MR2P 0-50 μ A., $1\frac{1}{2}$ " square, clear plastic	47/6

OA79 DIODES

Well known make. Brand New. 4/6 ea.

CRYSTAL MICROPHONES

Price only

52/6



Stand to suit
15/- extra.

Model BM3 (illustrated): Response 100-8,000 c/s,
fitted with 6 ft. cable and phone plug with on-
off switch. Can be used on stand for hand use.
BM3 Insert ... 10/- each

POWER CHOKES

12 Henrys, 125 mA., 275 Ohms, £2/8/0
12 Henrys, 100 mA., 290 Ohms, £1/12/0

CERAMIC CONDENSERS

Pigtail type. Sizes available: 1, 1.5, 2.2,
3.3, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22,
27, 29, 33, 39, 56, 68, 82, 100, 120, 150,
220, 270, 330, and 390 pF. 1/- each, or
24 for £1.

Q PLUS CHOKES

6 H. 175 mA. ... 20/-
10 H. 100 mA. ... 20/-

STEP-DOWN TRANSFORMER

New, 240/110 volts, 750 watts. £7/10/0.

ENGLISH INDICATOR UNITS TYPE 1

Contains: one 6" c.r. tube VCRX263,
three CV327/EF52, five CV858/EC91P/
6J6, two CV140/EB91/6AL5, and one
6V6GT. Brand new condition. £6/10/0.
5/- delivery charge to railroad.

MULTIMETER Model 200H

20,000 ohms per v. d.c. 10,000 ohms per v. a.c.



Specifications:
D.c. volts: 0-5, 25,
50, 250, 500, 2,500.
A.c. volts: 0-10, 50,
100, 250, 1,000.
D.c. current: 0-30
 μ A.; 25, 250 mA.
Resistance: 0-60K
ohms; 0-6 meg.
Capacity: 0.01-0.3
 μ F. (at a.c. 5v.);
0.001-0.01 μ F.
(at a.c. 250v.).
Decibel: minus 20
db. plus 22 db.
Output range: 0-10,
50, 100, 500, and
1,000.
Battery used: UM3
1.5v. 1 piece.
Dimensions: $3\frac{1}{4}$ x
 $4\frac{1}{2}$ x 1-1/8 in.

Complete with internal battery, testing leads
and prods.

Price £5/12/6 inc. tax.

Toggle Switches: d.p.d.t. 7/-, s.p.s.t. 6/-.

HAM RADIO SUPPLIERS

5A MELVILLE STREET, HAWTHORN, VICTORIA

Phone 86-6465

North Balwyn tram passes corner. Money Orders and Postal Notes payable North Hawthorn P.O. 5/- Packing Charge.

We sell and recommend Leader Test Equipment, Pioneer Stereo Equipment and Speakers, Hitachi Radio
Valves and Transistor Radios, Kew Brand Meters, A. & R. Transformers and Transistor Power Supplies,
Ducon Condensers, Welwyn Resistors, etc.

"AMATEUR RADIO"

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA. FOUNDED 1910.

JANUARY 1964

Vol. 32, No. 1

Editor:

K. M. COCKING VK3ZPQ

Publications Committee:

G. W. Baly (Secretary) VK3AOM
A. W. Chandler (Circulation) VK3LCL
S. T. Clark VK3ASC
R. S. Fisher VK3OM
R. W. Higginbotham VK3ERN
E. C. Manifold VK3EM
K. E. Pincoff VK3AFJ

Advertising Enquiries:

C/o P.O. Box 36, East Melbourne, C2, Vic.
OR
Mrs. BELLAIRS, Phone 41-3535, 478 Victoria
Parade, East Melbourne, C2, Victoria. Hours
10 a.m. to 3 p.m. only.

Publishers:

VICTORIAN DIVISION W.I.A.,
Reg. Office: 85a Franklin St., Melbourne, Vic.

Printers:

"RICHMOND CHRONICLE," Phone 42-3419.
Shakespeare Street, Richmond, E1, Vic.

★

All matters pertaining to "A.R." other
than subscriptions, should be addressed to:

THE EDITOR,
"AMATEUR RADIO,"
P.O. BOX 36,
EAST MELBOURNE, C2, VIC.

Acknowledgments will be sent following
the Committee meeting on the second Mon-
day of each month. All Sub-Editors should
forward their articles to reach "A.R."
before the 8th of each month. Any item
received after the Committee meeting will
be held over until the next month. Pub-
lication of any item is dependent upon space
availability, but in general about two
months may elapse before a technical
article is published after consideration by
the Publications Committee.

★

Members of the W.I.A. should refer all
enquiries regarding delivery of "A.R." direct
to their Divisional Secretary and not to
"A.R." direct. Non members of the W.I.A.
should write to the Victorian Division, C/o
P.O. Box 36, East Melbourne. Two months
notice is required before a change of mail-
ing address can be effected. Readers should
note that any change in the address of
their transmitting station must, by P.M.G.
regulation, be notified to the P.M.G. in the
State of residence, in addition "A.R." should
also be notified. A convenient form
is provided in the "Call Book".

★

Direct subscription rate is 24/- a year, post
paid, in advance. Issued monthly on the
first of the month, January edition excepted.

★

OUR COVER

An enlarged portion of a printed
circuit provides a modern style type
of painting for our January edition.
(Incidentally, all 1964 covers will be
a red colour to differentiate between
the 1963 (green) issues of "A.R.")

FEDERAL COMMENT

★

The commencement of another year is the usual time chosen for looking
to the future and injecting new ideas into an organisation such as ours.
This year of 1964 promises to be no exception to the rule. However, a
few comments of the previous Editorial are in order for it had not been
confirmed at that time what the final results of the Extraordinary Confer-
ence yielded. We are happy to confirm that the final Plenary meetings of
the Conference, dealing with frequency extensions for the Space Services,
preserved the status quo for the Amateur.

In Region 3, in which our particular interest lies, the Amateur band
144-148 Mc. is exclusively Amateur, and in addition a footnote has been
added to the effect that Amateurs may use artificial satellites for com-
munication purposes in this part of the band between 144-146 Mc. Our
delegate to the Conference, Mr. Tinkler, has now returned to Australia
and submitted a verbal report to Executive on his trip. A written report
will be published in this journal in the near future.

It is quite obvious from this report that the Amateurs would not have
fared as well as they did had it not been for the preliminary work and
exhausting discussions carried out by Amateurs with their administrations
prior to and during the Conference. One most important point arising from
this Conference appears to be the general feeling that future Conferences
will follow the lines of this one, in that it seems unlikely that a full scale
Conference such as the 1959 I.T.U. will continue in the future. They are
more likely to take the form of Conferences dealing with particular Services
such as the International Civil Aviation Organisation or Shipping.

This will mean shorter Conferences at more regular intervals because
it has been recognised that a period of four to five months at a Conference
is too long and too wearing on the nerves of the delegates. For this reason,
the foresight of Federal Council in deciding to immediately start collecting
funds was most timely. Some members have questioned the reasons for
requiring so much money to be raised by Divisions. It is the opinion of
Federal Council that a Fund must be set up in order to have representa-
tion as and when required. We may not be so fortunate in the future
as we have been in the past with our delegates who have had the backing
of their companies in regard to salaries and expenses.

The Amateur has now grown in stature in international affairs, but
in such growth must assume the responsibilities that it entails. He must
now consider himself an important part of an international brotherhood
which must be financially supported. It is certain that this subject will
receive a great deal of attention at the next Convention, but it appears
at this stage that an annual allotment from the membership subscription
should be set aside in a fund for the Amateur Service. Call this a fighting
fund if you wish, to protect our hobby, but despite its name, it should be
raised in the interests of the Amateur Service as a whole. This in turn
will mean greater co-operation between I.A.R.U. Societies, continual
liaison to appreciate one another's problems and a greater sense of
responsibility. This is the message then for the New Year—Let us all
assume our proper responsibilities as members of the Amateur Service
for a prosperous New Year.

FEDERAL EXECUTIVE, W.I.A.

CONTENTS

A Single Sideband System for 144 Mc.	2	Frequency Marker with 50 Kc. Intervals	21
Push-to-Talk on the Geloso G222TR Transmitter	3	John Moyle Memorial National Field Day Contest, 1964	15
Combination Measuring Unit for the Amateur Station	5	Australian DX Century Club Award	11
More About Crystals and Crystal Filters	7	Worked All VK Call Areas (W.A.V.K.C.A.) Award	11
Correspondence: Division of 420-450 Mc. Band	9	Australian D.X.C.C. Countries List Project Oscar	6
For the Beginner: A Simple Converter	10	Type F1 Emission	23
Recent Trends in Receiver Front-End Design	17	DX Notes	22
		SWL	24
		VHF	23

A SINGLE SIDEBAND SYSTEM FOR 144 Mc.

I. F. BERWICK,* VK3ALZ

It has long appeared to the writer that the ideal band on which to demonstrate the superiority of sideband for weak signal work is 144 Mc. Although it may take a little time for receivers to improve to the stage where the full 9 db. gain is realisable, it is hoped that the device presented here will pave the way towards that goal.

Despite the imposing title, this is a comparatively elementary device consisting of three parts—

1. A transmitting up converter.
2. An ABI driver stage.
3. A linear amplifier.

The design of such a converter calls for a little consideration. The problems are:—

- (a) Linearity of the s.b. amplifiers.
- (b) Spurious responses.
- (c) Stability of the oscillator.
- (d) Efficiency of mixer and amplifiers—an important consideration at 144 Mc.

It will be convenient to consider (a) and (d) in conjunction.

It transpires that some tube types which are highly suitable for mixer and amplifier service at h.f. on the grounds of linearity, are hopelessly inefficient at v.h.f.

The QE04/10 is a single ended beam tetrode on a B9G base and appears to be capable of good linearity and efficiency at 144 Mc.

SPURIOUS RESPONSES

Any given frequency, f_s , can be generated by mixing any other pair of frequencies, f_x and f_y , according to the formula:—

$$Z = X \pm Y.$$

However, certain combinations of X and Y will simplify the problem of suppression of the spurious responses.

Suppose we wish to obtain 144 Mc. s.b. We have available s.b. at the following frequencies: 4 Mc., 14 Mc., 50 Mc. Which frequency to choose?


We have—

- (a) $140 + 4 = 144$
 $140 - 4 = 136$
- (b) $148 - 4 = 144$
 $148 + 4 = 152$
- (c) $130 + 14 = 144$
 $130 - 14 = 116$
- (d) $158 - 14 = 144$
 $158 + 14 = 172$
- (e) $94 + 50 = 144$
 $94 - 50 = 44$
- (f) $194 - 50 = 144$
 $194 + 50 = 244$

Clearly—

- (a) and (b) are both unsatisfactory.
- (c) and (d) are both reasonably satisfactory.
- (e) is a quite popular scheme.
- (f) is highly satisfactory and is the scheme I have adopted.

(Continued on opposite page)

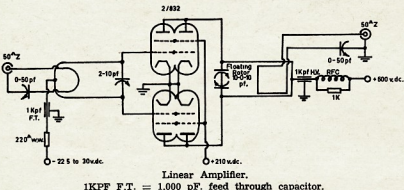

1KPF F.T. = 1,000 pF. feed through capacitor.

Clearly there is little reward in restricting the s.s.b. generator to a single band transmitter. One normally spends considerable time, not to mention expense, in developing an acceptable s.s.b. signal in the s.b. generator. It is highly desirable to use this acceptable signal on each band one normally operates. Hence the concept of the transmitting converter.

It is convenient, therefore, to investigate the linearity of tube types known to be efficient at 144 Mc.


It appears that certain deflection amplifiers have the desirable characteristics. Of these, the 12BY7 is probably the best. This tube is used extensively in commercial converters. I did not have this type available, but found the 6CK6 to be satisfactory. Of the other types used, the 5763 is satisfactory in Class A or ABI.

* 107 Loongana Avenue, Glenroy, Vic.

Transmitting Converter, 50 Mc. to 144 Mc.

Circuit continued on opposite page.

1KPF = 1,000 pF. feed through capacitor.

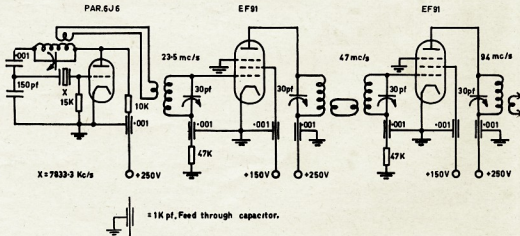

In this discussion it is assumed that both s.b. signal and the injection signal are free from spurious. The matter of spurious in the 50 Mc. transmitter was discussed in my previous article. An examination of the converter circuit will reveal that extensive measures have been adopted to eliminate spurious from the injection chain.

STABILITY OF THE OSCILLATOR

This is determined from the equation $x = 30 - \alpha$, where x c.p.s. is the required stability of the injection chain oscillator, and α c.p.s. is the overall stability of the s.b. source.

Since the practical aspects of oscillator stability have been adequately covered elsewhere and should be widely known, I do not propose to pursue this matter further.

LINEAR AMPLIFIER

The choice of tubes is strictly limited at 144 Mc. I have settled for a pair of 832As—not because they are the ideal tubes to use, but because they were available and efficient, and will satisfy the power requirement. They can also be replaced at a later date by the better QCE06/40s, with very minor circuit changes. The amplifier is identical with my 50 Mc. linear except that the coils are replaced with lecher bars and the negative feedback loop is omitted.

LINEARITY CHECKS

Despite what has been previously stated in this magazine and elsewhere, it appears that newcomers to s.b. (particularly the v.h.f. variety) imagine that a signal can be put on the air without any form of linearity check whatsoever. Any similarity between the resulting signal and s.b. can only be described as a remarkable coincidence.

Linearity checks are a must! If you don't have the necessary equipment to do the job, beg, buy or build it. The procedure for linearity checks is adequately covered in the Handbooks. ●


PUSH-TO-TALK ON THE GELOSO G222TR TRANSMITTER

BILL MAGNUSSON,* VK3AHT

THIS article will be of interest to all owners of the above transmitter. When operating in nets and contests one soon realises the shortcomings of a T/R switch that has to be reached for and rotated. I suppose the ultimate would be a foot operated switch and suspended mike or straight out vox. This article deals with p.t.t. but the problems encountered would be common to all three methods.

across the h.t. supply of the driver/sub-modulator. If this rotation is done fairly slowly the feedback and fade-away problem is eliminated, but if one is to use a relay here, circuit modifications must be made. That is unless you happen to have a relay with a wiping contact.

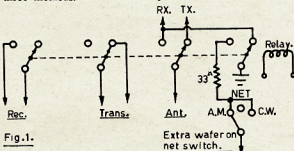The net signal also tends to linger. This is because the net switch does not provide this bleed.



The rather complicated switching system dictates the use of some sort of relay control. A close inspection of the circuit reveals several problems, however, and discloses the reasons for some of the odd habits of this transmitter.


Most users will have noticed that when listening on your own frequency there is a tendency for the carrier to linger for some seconds after switching from transmit to receive. This is annoying and is due to the power supply not having any permanent bleeds. This has been overcome (to a degree) in the original circuit by using a wiping contact on the T/R switch which momentarily shorts a bleed resistor

By using a four-pole double-throw relay to switch antenna and h.t., and by installing an extra wafer on the net switch, we can achieve very fast p.t.t. operation. The relay is wired as in the diagram so that section A controls the receiver, section B controls the transmitter h.t., section C controls the antenna change-over, and section D inserts the bleed resistor across the appropriate power supply.

Now due to the fact that this power supply is brought into action in the net position, provision must be made to remove this short at the same time. This is done by salvaging a switch wafer and longer shaft for the net switch. Mine came from a wrecked Geloso v.f.o. By an amount of gentle

(Continued on Page 21)

* 359 Williamstown Rd., Yarraville, Vic.

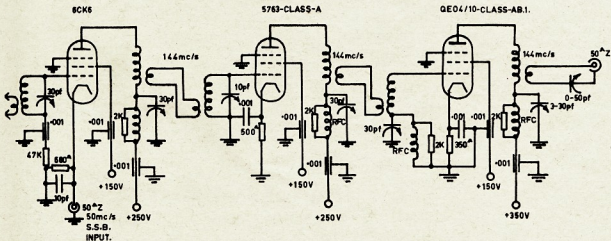

RADIO AMATEUR CALLBOOK

Radio Amateurs of the U.S.A. (all K and W calls). Listing over 240,000 Radio Amateurs in the 50 United States, its Possessions and personnel in foreign countries. Over 30,000 changes, including many thousand new licences, are made in each issue.

Price 52/6 (inc. postage)

Latest Edition.

FOREIGN RADIO AMATEUR CALLBOOK

Radio Amateurs outside of the U.S.A. Listing over 100,000 Radio Amateurs in all countries outside of the 50 United States. You will find in each issue thousands of new licensees and changes, gathered from every country of the world. Essential to DXers.

Price 32/6 (inc. postage)

Latest Edition.

RADIO AMATEUR DX GUIDE

Contains International DX Log, World and Prefix Maps, Great Circle Bearings, and many other features! Sixty-four pages of valuable information for Radio Amateurs everywhere! Crammed with maps, time conversion tables, and other data. Each 8½" x 12" page is easily removed for mounting under glass or on the wall.

Price 24/- (inc. postage)

Latest Edition.

INTERNATIONAL RADIO AMATEUR WORLD PREFIX MAP



This unabridged 29" x 42" Map, printed in four colours on heavy stock, shows Capitals and Major Cities of every land. At a glance, there are Radio Amateur Prefixes by Country, alphabetically-listed Prefixes, Countries and Continents, DX Zone Index, and World-wide Time Zones.

Price 26/3 post paid

THE RADIO AMATEUR'S WORLD ATLAS

Contains all six Continents of the world. West Indies-Caribbean area. Polar Projection of the world. Complete Country Prefix Index. 16 pages of 8½" x 12" on quality paper. Country Prefixes and Zone Boundaries on each map. Four beautiful colours. Only complete World Atlas compiled especially for Radio Amateurs. Continents are in the Lambert Azimuthal equal-area projection showing correct areas with minimum distortion. Price 26/3 post paid.

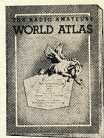


TABLE LAMPS

The latest thing for the shack. Large valves are mounted on 9" x 8" polished wooden base. A 40 watt lamp mounts inside antique map shade.

Price £5/10/0

P.-P. extra: N.S.W. 10/3, Qld. and Vic. 12/9; S.A., W.A., Tas., N.T. 16/9.

Please Note.—As the shape of the valves used varies considerably, the illustrations serve only as a guide to the general appearance of the lamp. Height of the lamps varies from 18 to 26 inches.



★ TUNING WANDS

An invaluable aid to resonating tuned circuits in Receivers and Transmitters, etc. Full details supplied with each Wand. Price 7/6 each

★ 85 Kc. I.F. TRANSFORMERS

Ex BC453 Command Receivers.

Three for 56/6 plus 3/- P.-P.

★ 2-15 pF. VARIABLE CONDENSERS

Ideal for v.h.f. gear, miniature variable condensers, ½" diam., ½" long shaft.

Two for 7/9 plus 2/- P.-P.

★ CARBON MICROPHONES

For Mobile use, Push-to-Talk Switch, provision to hang on dash board. New, complete with curly cord. 67/6 each, P. and P. 3/-.

★ CRYSTAL OVENS

Takes HC6/U Crystal, fits octal socket, 6.3v. at 0.85 amp., 75°C. 50/- each, P. and P. 2/-.

★ TUNING KNOB CRANKS

Ideal for moving from one end of the dial to the other end quickly. Fits 3/16" shaft. Could be made to fit onto large tuning knobs. 2 for 8/-, P. and P. 2/-.

★ 832, 4/20, 6/40 VALVE SOCKETS

Aluminium Recessed Valve Sockets, mica and ceramic insulation. 20/- each, P. and P. 2/-.

All goods despatched by Certified Mail. Be sure to include your full address and cheque or money order with your order.

PHONE OR MAIL ORDERS ONLY

NO CALLERS PLEASE

PHONE: XJ 6181, XJ 2353

TRANSTRONIC PRODUCTS

123 BALGOWLAH ROAD, FAIRLIGHT, N.S.W.

The same coils are used as with the g.d.o. They plug into an octal socket in the end of the box and are tuned by a 50 pF. air-spaced variable condenser mounted in the top of the box and fitted with an 180° scale; this can be directly calibrated.

The crystal diode CR1 is connected to the coil tap in order to obtain more efficient energy transfer between the high-impedance tuned circuit and the low impedance diode.

If a small aerial is plugged into J1, a standard coax socket, the unit will function as a Field Strength Indicator. And if a pair of high-impedance phones are plugged into J2, phone can be monitored.

For use as an Absorption Wavemeter, the unit is held with the coil near the tuned circuit under investigation and the 50 pF. variable condenser adjusted for maximum meter reading. The coupling should be kept to the minimum necessary to obtain a sharp reading, in order to minimise pulling between the two circuits.

If the instrument range switch is in the left hand position (see Fig. 1) a Grid Dip Oscillator may be plugged into the auxiliary socket.

GRID DIP OSCILLATOR

The Grid Dip Oscillator, shown on the left of the photograph uses a 6C4 in a Hartley circuit with plug-in coils.

The prototype was constructed in a 4" x 1½" x 1½" ex-A.M. pressed steel-case, but an Eddystone die-cast box would be more suitable.

The valve holder for the 6C4 is on an L-shaped bracket in the centre of the case, whilst an octal valve holder is mounted in the end of the case, to take the plug-in coils. The coils are wound on Denco ½" poly. octal plug-in formers for ranges 3-6. The coils for ranges 1-2 are on short lengths of 1" diameter paxolin tube glued into octal valve bases.

The tuned circuit is completed by a 50 pF. variable condenser mounted between the coil socket and the B7G valve holder. R.f. leads should be kept as short as possible for the v.h.f. range.

The sensitivity control R6, mounted on the main unit (see Fig. 1), controls the h.t. voltage to the oscillator. Some adjustment is necessary to compensate for variation of grid current with frequency, i.e. on change of band.

The g.d.o. will check the resonance of tuned circuits by noting the frequency at which a dip occurs in the grid current when the oscillator coil is coupled to an unknown circuit. It may also be used as a signal generator for testing receivers and converters. ●



"Well it looks a darned sight better without the call sign hovering above it."

PROJECT OSCAR

This is directed to all u.h.f. groups, club leaders, s.w.l.'s and the whole Amateur fraternity. Oscar III. will, it is hoped, go up in April 1964, so be in it.

Oscar III. will be a communications satellite, and some very good DX is expected from it, particularly on the u.h.f. bands. So chaps now is the time to organise in groups and be ready to report on it, and also to contact other Hams through it. It will have a power of some two and a half watts. Remembering that Oscar I. and II. had only 300 milliwatts, some £2 reports came from Australia and the islands. The top number of loggings made by any one Ham was 51. This was made by VK1VP, of Canberra. This is the sort of a report that is appreciated.

It is hoped that all States will select their State Co-ordinator now and go to it, letting all and sundry know about Oscar III. As news comes to hand, it will appear in this magazine, on W.I.A. broadcasts, and in the various Bulletins. There will, it is hoped, be a Oscar III network set up on 80 metres. You will have had some information in your State by now, so get cracking.

A model of Oscar will be on display in the various States soon, when we have found a way to get it around and at the same time cared for. No damage must befall this model as it has a long way to get yet.

Well chaps not too much more at this stage, see you later. May I take this opportunity to extend to all a very merry Xmas and a happy New Year.

—VK2HO, Co-ordinator.

POSTMASTER-GENERAL'S DEPARTMENT

has vacancies in Victoria for

RADIO TECHNICIANS

INSTALLATION — OPERATION — MAINTENANCE
V.H.F., U.H.F., AND MICROWAVE COMMUNICATION AND
TELEVISION LINK EQUIPMENT
BROADCASTING STUDIOS

Qualifications: Applicants should possess a good theoretical knowledge of Electronics combined with practical experience.

Conditions: Excellent working conditions, amenities and benefits, including paid sick leave and three weeks' annual leave. Some positions involve country travelling or shift work.

Salaries: £19/16/10 per week rising to £20/18/4 per week plus overtime and penalty rates.

Apply personally to:—

The Staff Employment Officer,
Lower Ground Floor, 250 Flinders Street, Melbourne.
Telephone: 60-4491.

W.I.A. D.X.C.C.

Listed below are the highest twelve members in each section. New members and those whose totals have been amended will also be shown.

PHONE

Call No.	Cer. Cnt-ries	Call No.	Cer. Cnt-ries
VK1MS	24 301	VK6KW	4 211
VK6RU	2 295	VK3WL	14 211
VK5AB	45 290	VK1ATN	25 204
VK5MK	43 294	VK4HR	12 192
VK3JAO	51 277	VK2JZ	61 190
VK4FJ	21 261	VK4RW	23 186

Amendment:

VK3TL 62 128

C.W.

Call No.	Cer. Cnt-ries	Call No.	Cer. Cnt-ries
VK3KB	10 316	VK2AGH	71 252
VK3CK	26 301	VK3RP	56 229
VK4FJ	29 286	VK3ARK	69 229
VK2QL	5 279	VK3PH	15 226
VK3NC	19 268	VK3BZ	6 222
VK6RU	18 256	VK3AK	23 220

Amendment:

VK2EO 2 209 VK3TL 78 149

OPEN

Call No.	Cer. Cnt-ries	Call No.	Cer. Cnt-ries
VK4RU	8 303	VK3HG	3 289
VK2ACK	6 300	VK3NC	77 269
VK4FJ	33 285	VK3JA	43 252
VK6MK	74 286	VK4HR	7 253
VK2AGH	83 286	VK3BZ	4 231
VK3JAO	76 280	VK3WL	45 225

Amendment:

VK3TL 85 182

MORE ABOUT CRYSTALS AND CRYSTAL FILTERS

ARIE BLES,* VK2AVA

EARLIER in 1963 I wrote some articles on FT241A low frequency crystals and high frequency filters using type FT243 crystals. In the course of several months of matching and adjusting crystals and filters, I have learned a few things worth mentioning.

FT241A TYPE CRYSTALS

If you have tried to either edge-grind them or silver-plate them for raising or lowering their frequencies, and have had the bad luck to break one or two of the suspension or contact wires, do not despair and throw that little rock away! In nine out of ten cases you can still fix your crystal to filter or oscillate, provided the little solder dots in the centre of the silver electrodes are still in position.

All you need to do is to find two thin strips of material, brass or tin-plate, to make two 1" long clips and to solder these to the crystal holder's pins. The strips must be flat and parallel, close together to hold the crystal between them, only touching the crystal at the two solder dots with a little pressure. Your crystal will be active again!



FT243 CRYSTALS

Most people do not possess the proper skill to grind these crystals for raising their frequencies. Etching with a saturated ammonium bi-fluoride solution is the easiest way. But if you need to shift the frequency more than say 100 kilocycles, you may already have a very transparent slab of crystal with extra smooth surfaces and the etching goes very slowly or stands almost still. Just heat your bi-fluoride solution to say 150 or more degrees (Fahrenheit), but do it in the open for the fluoride fumes are dangerous. The etching effect can thus be speeded up considerably.

What to do when you have gone too far in frequency? Well, if it is going to be a filter crystal, you can still lower the frequency as much as say 500 cycles by changing the pressure on the crystal electrodes in the holder, or by careful reduction of the little corners on the crystal electrodes, using a small honing stone.

If more frequency change is required it will be better to keep the crystal as an oscillator and use a different one for the filter.

More shift in frequency on active oscillator rocks can be achieved by weighting the crystal surfaces. Some use cold solder for that and rub it in. Personally, I prefer to use a soft pencil and rub a little carbon on the crystal. If you have applied too much (when the crystal stops oscillating, or if the frequency has been shifted too much) just wash the crystal in soap and water and start again.

Up to 1,500 to 2,000 cycles shift can sometimes be effected. I have never noticed that the frequency of a treated crystal drifted up again with time. Someone once said that he feared the carbon might be shedded again due to vibration of the crystal!

Of course one can also lower the frequency of a crystal as an oscillator

HIGHER FREQUENCY FILTERS

As I was playing with crystals for third overtone oscillator use, I started to wonder whether an active overtone crystal would perhaps also filter on or near that overtone frequency. And it does!

I have made up practical sets of filter crystals on 11 Mc., having a comparable bandwidth and shape factor as the filter sets on half that frequency. There is more work involved and much to be done on this project. Overtone crystals act differently from fundamental frequency ones and more careful adjustment is needed. But it works, and this can be a first example of such use of crystals.

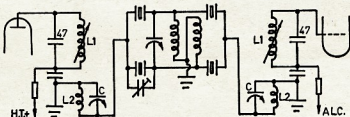


Fig. 1.

with a parallel capacity across it, but never expect more than 300 to 500 cycles shift in that manner. The crystal will stop oscillating with too much capacity across it.

HYBRID CRYSTAL FILTER CIRCUIT

The impedance of the h.f. crystal filter circuit published in Feb. and August issues of "A.R." is low and either a cathode follower input stage is recommended or some provision must be made to limit the influence of this low impedance loading on the rest of the circuit. In any case, the signal magnitude across a low impedance device is always small.

I have not seen a comment or attempt to overcome this in any magazine, and the solution given in Fig. 1 may really be a novelty.

For 5.5 to 6.0 Mc. operation, the input and output transformers can be made of 1" diameter t.v.-type 1:1 transformer forms. L1 is 45 turns, L2 is 15 turns, both close wound and only little spacing between the two coils. C is a 300/500 pF. mica compression trimmer. L1 is tuned to resonance with the former's iron slug, L2 with C, to give maximum output on the filter centre frequency.


The effect is amazing, the better impedance match between the filter and the high impedances of the input and output sides gives an extra good flat-topped filter passband and loads of signal at the grid of the following stage.

HARBROS TRANSISTOR POWER SUPPLIES


- ★ Any voltage to 1,000v. d.c. 400 mA.
- ★ Fully shielded and filtered.
- ★ Encapsulated Toroidal Transformers, Chokes, Transistors, etc.
- ★ Ex Stock at Manufacturers Prices.

Write for price on your individual requirements.

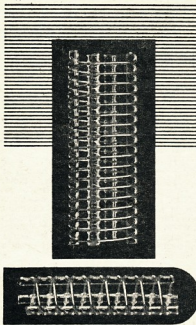B. HARDINGE & SONS
Healesville, Victoria
Phone 95



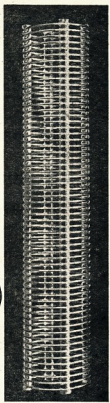ILLUMITRONIC ENGINEER. CORP.
California, U.S.A.



air dux

air-wound inductors

Illumitronic Engineering has developed a complete versatile series of air core inductors designed especially for the Amateur rig, for prototypes and production models of r.f. transmission equipment. These coils may be used for pi output circuits, conventional LC output circuits, interstage and oscillator circuits. The series consists of a standard coil type, a variable pitch type, an indented type and special wound type, in a range of diameters from $\frac{1}{4}$ inch to 5 inches. All Air Dux Coils are constructed of tinned or silver plated copper wire wound on large low-loss plastic rods for the highest mechanical strength and lowest electrical losses. Coils that resist heat distortion of temperatures up to 400°F. are available on special order for industrial and military use.

WRITE FOR FREE EIGHT-PAGE AIR DUX CATALOGUE

Australian Representatives:—

TRANSTRONIC PRODUCTS

123 BALGOWLAH ROAD, FAIRLIGHT, N.S.W.

Phone: 94-6181

A complete range of these Coils are also available from:—

Victoria:

J. M. MAGRATH & CO. P/L
208 Lt. Longdale St., Melbourne
Phone: 32-3731

Queensland:

C. A. PEARCE PTY. LTD.
33 Bowen Street, Brisbane
Phone: 2-8510

FOSTER DYNAMIC MICROPHONES

SPECIFICATIONS:

Output Impedance	50 ohms or 50K ohms
Effective output level —55 db. [0 db. — (one) 1V. Microbar]	
Frequency response	50 to 15,000 c.p.s.


OMNI-DIRECTIONAL DYNAMIC:

Plastic Diaphragm.	Swivel fits 5/8" 26 t.p.i. Stands.
Size: 4½" long, 1½" diameter.	Colour: TWO-TONE GREY.
Cable: 12 ft. of P.V.C.	

Retail Price 50 ohms: £4/7/9 + Sales Tax 10/11

Retail Price 50K ohms: £4/10/0 + Sales Tax 11/3

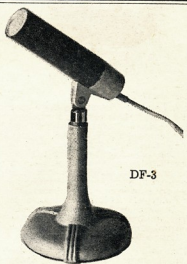A QUALITY PRODUCT FOR TAPE RECORDERS & P.A. USERS



DF-3



Marketed by **ZEPHYR PRODUCTS PTY. LTD.**

58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA

Phones: 25-1300, 25-4556

Manufacturers of Radio and Electrical Equipment and Components

Agents: D. K. Northover & Co.; Neil Muller Ltd.; Homecrafts (Tas.) P/L; Jacoby, Mitchell & Co. P/L; T. H. Martin P/L.

DIVISION OF 420-450 Mc. BAND

Editor "A.R.,"

Dear Sir,

With the eminent opening of the 420-450 Mc. band to Amateurs, the incentive to undertake some of the less common modes of transmission (particularly t.v. and f.m.) will be greatly increased. To try to cope with the problem of standard frequencies and channels to fit in with possibly existing equipment, I should like to submit the following for consideration by all Amateurs.

- (1) The band 420-450 Mc. is wide enough to accommodate four channels, each 7 Mc. wide, for Amateur T.V., but to leave sufficient bandwidth for guard bands and other services, and to fit in with the standard domestic t.v. receiver which would most probably be the common method of reception, only three channels are envisaged.
- (2) In considering the domestic t.v. receiver (which would most probably be used as a tuneable i.f. to save modification) note must be taken that the use of the high band channels as the first i.f. would most likely add to the already difficult problem of converter noise at 420 Mc., and therefore the use of the low band is recommended. However, in the low band there are no three adjacent channels which would be the most convenient to use, but as channels 4 and 5 are adjacent, and channel 3 is spaced only 2 Mc. away, it would suggest the use of channels 3, 4 and 5 as the i.f., i.e. from 85 to 108 Mc., and this presupposes the use of a converter with local oscillator injection at 340 Mc.

Now to consider the placement of these bands within the 420-450 Mc. band. As has been seen on the majority of other v.h.f. bands, the majority of serious a.m., c.w. and s.s.b. operating is confined to the lower edges of the band, then it would seem logical to have the three t.v. channels at the top end of the band. Here though rises the problem of a guard band to reduce the possibility of out-of-band operation, and if consideration is given to the many possible d.s.b., i.e. non vestigial sideband transmissions which will most likely be undertaken, a minimum guard band of 2 Mc. is suggested.

This now leaves us with the following channeling:—

- (1) 420-425 Mc.—a.m., s.s.b., c.w.
- (2) 425-432 Mc.—a.t.v. ch. 1 (ch. 3 on t.v. rx).
- (3) 432-434 Mc.
- (4) 434-441 Mc.—a.t.v. ch. 2 (ch. 4 on t.v. rx).
- (5) 441-448 Mc.—a.t.v. ch. 3 (ch. 5 on t.v. rx).
- (6) 448-450 Mc.—guard band.

Now two further advantages immediately become obvious.

(a) Using a converter with 340 Mc. injection, the band 428-448 Mc. is converted to 88-108 Mc., i.e. the coverage of a standard f.m. v.h.f. receiver, many of which are still owned by Amateurs, and which are still available in many overseas equipments.

(b) The band 432-434 Mc. which lies between two t.v. channels is exactly three times 144.0 to 144.6 Mc., thus enabling the operators of many 2 metre transmitters to triple directly using existing transmitters and crystals. However, the first 5 Mc. has already been suggested for the more common modes, and therefore it is suggested that only 1 Mc. be available to these modes, e.g. from 432-433 Mc., the remainder from 433-434 Mc. being only for wide-band f.m. as this portion would be covered by the standard f.m. tuner.

In fact another point now arises. Many Amateurs when starting t.v. transmissions will not have the facilities for intercarrier sound, and then these two channels become eminently suitable for use as the accompanying sound channels for t.v. transmission without intercarrier sound. Intercarrier sound would normally be available through the standard t.v. receiver.

A further look at the Amateur t.v. position will show that many Amateurs wishing to commence video transmissions will wish to use double sideband

as being the easiest to generate. Therefore, to prevent any interference with any other services, the a.t.v. ch. 3 of 441-448 Mc. could be used for double sideband, the unused or lower sideband then falling in the 434-441 Mc. of a.t.v. ch. 2 band. Therefore a.t.v. ch. 1, 425-432 Mc., should be reserved only for vestigial sideband transmissions with intercarrier sound as conforming to P.M.G. and C.C.I.R., and it is suggested that all official transmissions, e.g. W.I.A. etc., take place on this channel.

It is obvious that people wishing to do serious a.m., c.w. and s.s.b. work would build special narrow band converters to feed into their own communications receivers, but for persons wishing to experiment with t.v. the band resolves as follows:—

- (1) 420-425 Mc.—a.m., s.s.b., c.w. etc. (narrow band).
- (2) 425-432 Mc.—a.t.v. ch. 1, vestigial sideband, intercarrier sound, full C.C.I.R. specs. only.
- (3) 432-433 Mc.—a.m., sound associated with video transmissions in a.t.v. ch. 2 and 3, non-intercarrier.
- (4) 433-434 Mc.—wide band f.m., sound associated with video transmissions in a.t.v. chs. 2 and 3, non-intercarrier.
- (5) 434-441 Mc.—a.t.v. ch. 2, vestigial sideband only, intercarrier f.m. sound or non-intercarrier a.m. or f.m. as in (3) and (4).
- (6) 441-448 Mc.—a.t.v. ch. 3, vestigial or double sideband video, intercarrier f.m. sound or non-intercarrier a.m. or f.m. as in (3) and (4).
- (7) 448-450 Mc.—guard band to prevent out-of-band t.v. signals, but may be used for other narrow band modes if so desired.

These allocations are shown diagrammatically and will assist in an understanding. It would be most opportune if all Amateurs could consider these proposals and advise their local W.I.A. Divisions so that some form of gentleman's agreement may be formulated.

Incidentally, for those interested in building wide band converters with 340 Mc. injection as suggested, quartz crystals on 37.7778 Mc. (one-ninth of 340 Mc.) are being advertised in "Wireless World" by Henry's Radio at 7/6 sterling.

—Douglas W. Rickard, VK2ZDI.




PRINTED CIRCUITS FOR CARS

A British car manufacturer has announced that a new model car they will be producing will use a printed circuit wiring panel behind the dashboard. This will eliminate the familiar wiring harness with its multitude of leads.



NOW REASONABLY WELL

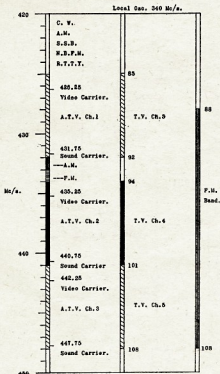Bill Barber, VK5DX, in a note to the Editor, sends his regards to all Amateurs and mentions that although he has not been in the best of health for the past two years, he is now reasonably well.



A SIMPLE CONVERTER

WITH the advent of Y.R.C.'s I frequently hear demands for a simple converter. Such a converter has been described for a number of years in the A.R.R.L. Handbook. It is very inexpensive and can be used with practically any broadcast receiver, preferably those without a ferrite antenna stick system. The necessary power outlet could be fitted on a broadcast receiver under the supervision of the Y.R.C. leader and if necessary an aerial terminal.

Why is it inexpensive? The band-setting for 3.5 Mc. or 7.0 Mc. is by a two-gang capacitor about 365 pF. from any old scrapped radio. Band-tuning by 15 pF. capacitor (two for 7/9 advertised in "A.R."), one valve 6U8, one coil only (for the two bands, no switch). About a dozen resistors and condensers and, of course, the advantage that the bands are bandspread around 100° of the tuning dial.

For those who have not access to a A.R.R.L. Handbook, here is a brief description and circuit.

L1 couples aerial to L2. L2 and L3 form a bandpass circuit that can be tuned by the two gang (C1A and C1B) to 3.5 Mc. or 7.0 Mc. This bandpass circuit is coupled to the pentode section of the 6U8, acting as a mixer. In the anode circuit of the mixer is L6 and C7, tuned to 1700 kc., and L7 is coupled to the broadcast receiver.

L4, L5, C2 and C3, controlled from the panel, forms the main tuning. The oscillator tunes from 5.2 Mc. to 5.7 Mc. (Any Amateur would set this range for intending constructors.) Thus with this range the oscillator is 1700 kc. difference from the signal on 3.5-4.0 Mc. and 1700 kc. difference from 6.9 Mc. to 7.4 Mc. Thus which band appears as an i.f. of 1700 kc. will depend purely on the setting of the two-gang.

Note: The two-gang capacitor must be insulated from the chassis.

There are only two panel controls, a small knob on the two-gang termed "band set" and a slow motion device labelled "bandspread". If a slow motion

dial is not available, a cord drum from a scrapped radio driven by a rubber grommet on a $\frac{1}{4}$ " shaft makes an ideal replacement. A cardboard scale can be glued to the drum and an old volume control with the wiper gear cut away makes a good panel mount for the grommet spindle. A s.a.c. answers any queries or assistance to constructors.

Coil data (all coils 1" diameter):

L1—8 turns 22 s.w.g., $\frac{1}{4}$ " long.



L2—19 turns 22 s.w.g., 19/32" long.

L3—Same as L2.

L4—21 turns 22 s.w.g., 21/32" long.

L5—8 turns 22 s.w.g., $\frac{1}{4}$ " long.

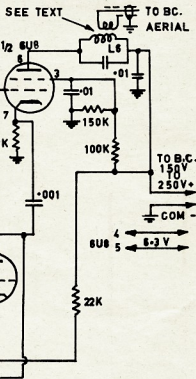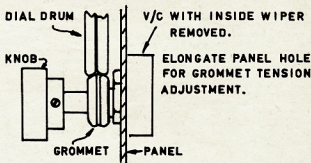L1 is separated from L2 by 1/32" and wound on the same former. L4 and



L5 are separated by 1/32" and wound on same former.

Coils L1 and L2 should be mounted at right angles to L3.

The i.f. coils L6 and L7 can be a variety of arrangements:—

(1) 50-60 turns 28-32 s.w.g., paralleled with a 600 pF. capacitor and coupling winding of 20 turns wound on the cold end; 3/8" diameter slug tuned former.

(2) A r.f. choke of the all-wave type about 4 or 5 pies, and about 20 turns 28-32 s.w.g. wound near the cold end; no parallel capacitor with the choke.

(3) As for (2), but instead of a coupling winding, a 100 pF. condenser from the top or anode end to the b.c. set aerial terminal.

(4) The medium wave oscillator coil from a scrapped radio with a coupling winding of 20-30 turns added, or if a cathode tap of 100 pF. to b.c. set

Whichever course is adopted it must be fitted in a screened box or can, and of course to prevent b.c. break-through the whole should be in a metal box, a half size biscuit tin would make a good enclosure, or one of the aluminium or tin plate baking dishes sold in the multiple stores would do.

—A. F. W. Haddrell, VK3ZFC

(This circuit originally appeared in the A.R.R.L. Handbook.)

AUSTRALIAN DX CENTURY CLUB AWARD

OBJECTS

1. This Award was created in order to stimulate interest in working DX in Australia and to give successful applicants some tangible recognition of their achievements.
2. This Award, to be known as the "DX Century Club" Award, will be issued to any Australian Amateur who satisfies the following conditions.
3. A certificate of the Award will be issued to the applicants who show proof of having contacted one hundred countries, and will be endorsed as necessary, for contacts made using only one type of emission.

REQUIREMENTS

1. Verifications are required from one hundred different countries as shown in the Official Countries List.
2. The Official Countries List will be published annually in "Amateur Radio" and will be amended from time to time as required. Should a country be deleted from the Countries List at any time, members and intending members will be credited with such country if the date of contact was before such deletion.
3. The commencing date for the Award is 1st January 1946. All contacts made on or after this date may be included.

OPERATION

- 3.1. Contacts must be made in the H.F. Band (Band 7) which extends from 3 to 30 Mc., but such contacts must only be made in the authorised Amateur Bands in Band 7.

- 3.2. All contacts must be two-way contacts on the same band. Cross band contacts will not be allowed.
- 3.3. Contacts may be made using any authorised type of emission for the band concerned.
- 3.4. Credit may only be claimed for contacts with stations using regularly-assigned Government call signs for the country concerned.
- 3.5. Contacts made with ship or aircraft stations will not be allowed, but land-mobile stations may be claimed provided their specific location at the time of contact is clearly shown on the verification.
- 3.6. All stations must be contacted from the same call area by the applicant, although if the call sign is subsequently changed, contact will be allowed under the new call sign providing the applicant is still in the same call area.
- 3.7. All contacts must be made when operating in accordance with the Regulations laid down in the "Handbook for the Guidance of Operators of Amateur Wireless Stations" or its successor.

VERIFICATIONS

- 4.1. It will be necessary for the applicant to produce verifications in the form of QSL cards or other written evidence showing that two-way contacts have taken place.
- 4.2. Each verification submitted must be exactly as received from the station contacted, and altered or forged verifications will be grounds for disqualification of the applicant.

- 4.3. Each verification submitted must show the date and time of contact, type of emission and frequency band used, the report and the location or address of the station at the time of contact.
- 4.4. A check list must accompany every application setting out the details for each claimed station in accordance with the details required in Rule 4.3.

APPLICATIONS

- 5.1. Applications for membership shall be addressed to the Awards Officer, Box 2611W, G.P.O., Melbourne, Vic., accompanied by the verifications and the check list with sufficient postage enclosed for their return to the applicant, registration being included if desired.
- 5.2. A nominal charge of 2/6, which shall also be forwarded with the application, will be made for the issue of the certificate to successful applicants who are non-members of the Wireless Institute of Australia.
- 5.3. Successful applicants will be listed periodically in "Amateur Radio". Members of the D.X.C.C. wishing to have their verified country totals, over and above the one hundred necessary for membership, listed will notify these totals to the Awards Officer.
- 5.4. In cases of dispute, the decision of the Awards Officer and two members of the Federal Executive of the W.I.A. in the interpretation and application of these Rules shall be final and binding.
- 5.5. Notwithstanding anything to the contrary in these Rules, the Federal Council of the W.I.A. reserves the right to amend them when necessary.

WORKED ALL VK CALL AREAS (W.A.VK.C.A.) AWARD

OBJECTS

1. This Award, to be known as the W.A.VK.C.A. Award, is offered by the Wireless Institute of Australia as tangible evidence of the proficiency of overseas Amateurs in making contacts with the various call areas of the Commonwealth of Australia.
2. The Award may be claimed by any Amateur in the world who is a member of an affiliated Society of the I.A.R.U., but no Australian Amateur will be eligible.

REQUIREMENTS

- 2.1. A handsome Certificate will be awarded to any applicant who makes contacts with Australian Amateur Stations in the areas shown in the attached Appendix. The number of contacts required in each area is also shown.
- 2.2. In the case of applications prior to 1st January, 1964, a total of three (3) confirmations will suffice for VK1 and VK2; thereafter one confirmation for Australian Capital Territory (VK1) will be necessary as shown in the Appendix.

OPERATION

- 3.1. Contacts between overseas stations and Australian stations must have been made on or after the 1st January, 1946.
- 3.2. Contacts may be made using any authorised frequency band or type of emission permitted to Australian Amateurs, but cross band contacts will not be allowed.
- 3.3. No contacts made with ship or aircraft stations in Australian territories will be eligible, but land-mobile or portable stations may be contacted provided the location at the time of contact is shown on the confirmation.

VERIFICATIONS

- 4.1. The applicant must submit documentary proof, in the form of QSL cards or other written evidence, confirming that two-way contacts have taken place. Such verifications must show the date and time of contact, type of emission and frequency used, signal reports and location (in the case of portable or land-mobile operation) of the stations contacted.
- 4.2. Verifications must be submitted exactly as received, and forged or altered evidence may result in the disqualification of the station concerned.
- 4.3. A list, in accordance with the details required in Rule 4.1, must be submitted with the application for the Award.

APPLICATIONS

- 5.1. All claims for the W.A.VK.C.A. Award must be made by the submission of the confirmations (Rule 2.1 or 2.2), together with the list (Rule 4.3), direct to "Awards Manager," Box 2611W, G.P.O., Melbourne, Australia. Sufficient International Reply Coupons must be enclosed to cover return postage of the confirmations to the applicant.
- 5.2. Where a reciprocal agreement exists between the W.I.A. and the applicant's Society, the appointed officer of that Society will carry out the check, and if correct, will forward a written application for the Award on behalf of the applicant, together with the list (Rule 4.3).
- 5.3. Applications will be examined by the Awards Manager, who will arrange for the Award to be forwarded either direct or through the applicant's Society. The Awards Manager's decision on the application and interpretation of these Rules will be final and binding.

- 5.4. Notwithstanding anything in the Rules to the contrary, the Federal Council of the W.I.A. reserves the right to amend these Rules as necessary.

APPENDIX

Territory	Call Area	QSLs Required
Australian Antarctica
Heard Island	...	VK0 1
Macquarie Island
Australian Capital Territory	...	VK1 1
Lord Howe Island
State of New South Wales	...	VK2 3
State of Victoria	...	VK3 3
State of Queensland
Thursday Island	...	VK4 3
Willis Island
State of South Australia	...	VK5 3
State of Western Australia	...	VK6 3
Flinders Island
King Island	...	VK7 3
State of Tasmania
Northern Territory	...	VK8 1
Admiralty Islands
Bougainville Island
Christmas Island
Cocos Islands
Nauru	...	VK9 1
New Britain
New Guinea
New Ireland
Norfolk Island
Papua Territory

Note.—In Areas above, where more than one confirmation is required, contacts may be made with any or all of the Territories listed in brackets.

AUSTRALIAN D.X.C.C. COUNTRIES LIST

	Phone	C.W.		Phone	C.W.
AC3	Sikkim		FK8	New Caledonia	
AC4	Tibet		FL8	Fr. Somaliland	
AC5	Bhutan		FM7	Martinique	
AP	East Pakistan		FN	(prior 1/11/54) French India	
AP	West Pakistan		FO8	Clipperton I.	
BV (C3)	Formosa		FO8	Fr. Oceania	
BY (C)	China		FP8	St. Pierre & Miq. Is.	
C9	Manchuria		*FQ8	Fr. Equatorial Africa	
CE	Chile		TL8	(fr. 13/8/60) Cen. Afric. R.	
CE9, KC4, LU-Z, VK0, VP8, ZL5	etc., Antarctica		TN8	(from 15/8/60) Congo Rep.	
CE0A	Easter I.		TR8	(from 17/8/60) Gabon Rep.	
CE0Z	J. Fernandez Arch.		TT8	(from 11/8/60) Chad Rep.	
CM, CO	Cuba		FR7	(from 25/6/60) Glorioso I.	
CN2 (prior 1/7/60)	Tangier		FR7	(from 25/6/60) Juan de Nova	
CN2, 8, 9	Morocco			and Europa Is.	
CP	Bolivia		FR7	Reunion I.	
CR4	Cape Verde Is.		FR7	Tromelin Is.	
CR5	Portuguese Guinea		FS7	Saint Martin	
CR5	Principe, Sao Thome		FU8, YJ1	New Hebrides	
CR6	Angola		FW8	Wallis & Futuna Is.	
CR7	Mozambique		FY7	Fr. Guiana & Inini	
CR8 (prior 1/1/62)	Goa		G	England	
CR8	Port. Timor		GC	Guernsey and Deps.	
CR9	Macao		GC	Jersey I.	
CT1	Portugal		GD	Isle of Man	
CT2	Azores		GI	Northern Ireland	
CT3	Madeira Is.		GM	Scotland	
CX	Uruguay		GW	Wales	
DJ, DL, DM	Germany		HA	Hungary	
DU	Philippine Is.		HB	Switzerland	
EA	Spain		HC	Ecuador	
EA6	Balearic Is.		HC8	Galapagos Is.	
EA8	Canary Is.		HE	Liechtenstein	
EA9	Ini		HH	Haiti	
EA9	Rio de Oro		HI	Dominican Rep.	
EA9	Spanish Morocco		HK	Colombia	
EA0	Spanish Guinea		HK0	Arch. of San Andres	
EI	Rep. of Ireland			and Providencia	
EL	Liberia		HK0	Bajo Nuevo	
EP, EQ	Iran		HK0	Malpeho Is.	
ET2 (prior 14/11/62)	Eritrea		HL, HM, 6N5	Korea	
ET2, 3	Ethiopia		HP	Panama	
F	France		HR	Honduras	
FB8	A'dam & St. Paul Is.		HS	Thailand	
FB8	Kerguelen Is.		HV	Vatican	
FC	Corsica		HZ	Saudi Arabia	
*FF8	French West Africa		I1, IT1	Italy	
TU2 (fr. 7/8/60)	Ivory Coast R.		I1	(prior 1/4/57) Trieste	
TY2 (fr. 1/8/60)	Dahomey Rep.		I5	(prior 1/7/60) It. Somaliland	
TZ2 (from 20/6/60)	Mali Rep.		IS1	Sardinia	
XT2 (from 5/8/60)	Voltaic Rep.		JA, KA	Japan	
5U7 (from 3/8/60)	Niger Rep.		JT1	Mongolia	
5T5 (from 20/6/60)	Mauritania		JY	Jordan	
6W8 (fr. 20/6/60)	Senegal Rep.		JZ0	(pr'r 1/5/63) W. New Guinea	
FG7	Guadeloupe		K, W	U.S.A.	
FH8	Comoro Is.		KA0, KG6I	Bonin & Volcano Is.	
FI8 (pr'r 20/7/55)	Fr. Indo China		KB6	Baker, Howland and	
				Am. Phoenix I. (Inc. Canton I.)	

* Fr. West Africa and Fr. Equatorial Africa: Only contacts dated prior to when the particular area obtained separate listing (as shown) will count.

	Phone	C.W.		Phone	C.W.
KC4	Navassa I.		ST2	Sudan	
KC6	Eastern Caroline Is.		SU	Egypt	
KC6	Western Caroline Is.		SV	Crete	
KG4	Guantanamo Bay		SV	Dodecanese	
KG6	Guam		SV	Greece	
KG6	Marcus I.		TA	Turkey	
KG6 (Rota, Tinian, Saipan, etc.)			TF	Iceland	
	Mariana Is.		TG	Guatemala	
KH6	Hawaiian Is.		TI	Costa Rica	
KH6	Kure I.		TI9	Cocos I.	
KJ6	Johnston I.		TJ (F8)	Cameroon Rep.	
KL7	Alaska		TL, TN, TR, TT (see after FQ8)		
KM6	Midway Is.		TS (3V8)	Tunisia	
KP4	Puerto Rico		TU, TY, TZ (see after FF8)		
KP6	Palmyra Group, Jarvis I.		UA1-6, UN1	Eur. R.S.F.S.R.	
KR6	Ryukyu Is.		UA1	Franz Josef Land	
KS4B	Serrana Bank and Roncador Cay		UA2	Kaliningrad Region	
KS4	Swan Is.		UA9, 0	Asiatic R.S.F.S.R.	
KS6	American Samoa		UA0 (prior 1/9/60)	Wrangel I.	
KV4	Virgin Is.		UB5	Ukraine	
KW6	Wake I.		UC2	White Russian S.S.R.	
KX6	Marshall Is.		UD6	Azerbaijan	
KZ5	Canal Zone		UF6	Georgia	
LA	Bouvet I.		UG6	Armenia	
LA	Jan Mayen		UH8	Turkoman	
LA	Norway		UI8	Uzbek	
LA	Svalbard		UJ8	Tadzhik	
LU	Argentina		UL7	Kazakh	
LX	Luxembourg		UM8	Kirghiz	
LZ	Bulgaria		UN1 (prior 1/7/60)	Kar-Fin.Rep.	
MP4	Bahrain		UO5	Moldavia	
MP4	Qatar		UP2	Lithuania	
MP4	Trucial Oman		UQ2	Latvia	
OA	Peru		UR2	Estonia	
OD5	Lebanon		VE, VO	Canada	
OE	Austria		VK	Australia	
OH	Finland		VK2	Lord Howe Is.	
OH0	Aland Is.		VK4	Willis Is.	
OK	Czechoslovakia		VK9	Christmas I.	
ON4	Belgium		VK9	Cocos Is.	
OX, KG1	Greenland		VK9	Nauru I.	
OY	Faeroes		VK9	Norfolk I.	
OZ	Denmark		VK9	Papua Terr.	
PA0, PI1	Netherlands		VK9	Terr. of New Guinea	
PJ	Neth. West Indies		VK0	Heard I.	
PJ2M	Sint Maarten		VK0	Macquarie I.	
PK (from 1/5/63)	Indonesia		VO (prior 1/4/49)	Newf./Lab.	
PK1, 2, 3 (prior 1/5/63)	Java		VP1	British Honduras	
PK4 (prior 1/5/63)	Sumatra		VP2 (prior 1/6/58)	Leeward Is.	
PK5 (prior 1/5/63)	Borneo		VP2	Anguilla	
PK6 (prior 1/5/63)	Celebes and Molucca Is.		VP2	Antigua, Barbuda	
PX	Andorra		VP2	Br. Virgin Is.	
PY	Brazil		VP2	Montserrat	
PY0	Fernando de Noronha		VP2	St. Kitts, Nevis	
PY0	Trindade & Martin Vaz Is.		VP2 (prior 1/6/58)	Windw'd Is.	
PZ1	Netherlands Guiana		VP2	Dominica	
SD1 (ZS7)	Swaziland		VP2	Grenada & Deps.	
SL, SM	Sweden		VP2	St. Lucia	
SP	Poland		VP2	St. Vincent & Deps.	
			VP3	British Guiana	
			VP4	Trinidad & Tobago	

† One contact with each group formerly known as "Leeward Is." and "Windward Is." dated prior to 1/6/58 may be credited, in which case no further credit as a separate listing, as from 1/6/58, will be given those particular islands.

	Phone	C.W.		Phone	C.W.
VP5	Cayman Is.		ZD3	Gambia	
VP5	Turks & Caicos Is.		ZD4 (prior 5/3/57)	Gold Coast,	
VP6	Barbados			Togoland	
VP7	Bahama Is.		ZD6	Nyasaland	
VP8	Falkland Is.		ZD7	St. Helena	
VP8, LU-Z	South Georgia		ZD8	Ascension Is.	
VP8, LU-Z	South Orkney Is.		ZD9	Tristan da Cunha and	
VP8, LU-Z	South Sandwich Is.			Gough I.	
VP8, LU-Z, CE9	Sth. Shet. Is.		ZE	Southern Rhodesia	
VP9	Bermuda Is.		ZK1	Cook Is.	
VQ1	Zanzibar		ZK1	Manihiki Is.	
VQ2	Northern Rhodesia		ZK2	Niue	
VQ6 (prior 1/7/60)	Br. Somali'd		ZL	Chatham Is.	
VQ8	Cargados Carajos Shs.		ZL	New Zealand	
VQ8	Chagos Is.		ZL1	Kermadec Is.	
VQ8	Mauritius		ZL4	Auckland and Campbell Is.	
VQ8	Rodriguez I.		ZM7	Tokelau	
VQ9	Aldabra Is.		ZP	Paraguay	
VQ9	Seychelles		ZS1, 2, 4, 5, 6	Rep. of S. Africa	
VR1 (includ. Canton Is.)	British		ZS2	Prince Ed. and Marlon I.	
	Phoenix Is.		ZS3	South-West Africa	
VR1	Gilbert & Ellice Is.		ZS7 (see SD1)		
	and Ocean I.		ZS8	Basutoland	
VR2	Fiji Is.		ZS9	Bechuanaland	
VR3	Fanning & Christmas Is.		3A	Monaco	
VR4	Solomon Is.		3W8, XV5	Vietnam	
VR5	Tonga Is.		4S7	Ceylon	
VR6	Pitcairn I.		4W1	Yemen	
VS1 (prior 16/9/63)	Singapore		4X4 (from 14/5/48)	Israel	
VS1, 9M2 (from 16/9/63)	West		5A	Libya	
	Malaysia		5B4	Cyprus	
VS4, ZC5 (from 16/9/63)	East		5H3	Tanganyika	
	Malaysia		5N2	Nigeria	
VS4 (prior 16/9/63)	Sarawak		5R8	(Madagascar) Malagasy	
VS5	Brunei		5T5 (see after FF8)		
VS6	Hong Kong		5U7 (see after FF8)		
VS9	Aden & Socotra		5V	Togo Rep.	
VS9	Kamran Is.		5W1 (ZM6)	Samoa	
VS9	Kuria Muria		5X5 (VQ5)	Uganda	
VS9	Maldiva Is.		5Z4 (VQ4)	Kenya	
VS9	Sultanate of Oman		6N5 (see HL)		
VU2	India		6O1, 6O2 (from 1/7/60)		
VU...	Laccadive Is.			Somalia Rep.	
VU	Andaman & Nicobar Is.		6W8 (see after FF8)		
XE, XF	Mexico		6Y (VP5)	Jamaica	
XE4	Revilla Gigedo		7G1 (from 1/10/58)	Rp. of Guinea	
XT2 (see after FF8)			7X2 (FA)	Algeria	
XW8	Laos		9A (MI)	San Marino	
XZ2	Burma		9G1 (from 5/3/57)	Ghana	
YA	Afghanistan		9K2	Kuwait	
YI	Irak		9K3	Kuwait-Saudi Arabia N.Z.	
YK	Syria		9L1 (ZD1)	Sierra Leone	
YN, YN0	Nicaragua		9M2 (prior 16/9/63)	Malaya	
YO	Roumania		9N1	Nepal	
YS	Salvador		9Q5 (previously OQ5-0)	Rep. of	
YU	Yugoslavia			The Congo	
YV	Venezuela		9S4 (prior 1/4/57)	Saar	
YV0	Aves I.		9U5 (from 1/7/60 to 30/6/62)		
ZA	Albania			Ruanda-Urundi	
ZB1	Malta		9U5 (from 1/7/62)	Rwanda Rep.	
ZB2	Gibraltar		9X5 (from 1/7/62)	Burundi	
ZC5 (pr. 16/9/63)	Br. Nth. Borneo		—	Cambodia	
ZC6	Palestine				

JOHN MOYLE MEMORIAL NATIONAL FIELD DAY CONTEST, 1964

Saturday, 8th February, to Sunday, 9th February

DATE

Saturday, 8th February, to Sunday, 9th February, 1964.

DURATION

From 1600 hours E.A.S.T., 8th February, to 1600 hours E.A.S.T., 9th February, 1964.

OBJECTS

The operators of Portable and Mobile Stations within all VK Call Areas will endeavour to contact other Portable/Mobile and Fixed Stations in Australian and Overseas Call Areas.

RULES

1. There shall be five sections in the Contest:—

- (a) Portable/Mobile Transmitting, Phone.
- (b) Portable/Mobile Transmitting, C.W.
- (c) Portable/Mobile Transmitting, Multiple Operators, Open only.
- (d) Fixed Transmitting Stations working Portable/Mobile Stations, Open only.
- (e) Reception of Portable/Mobile Stations.

2. All Australian Amateurs may take part. Mobile or Portable Stations shall be limited to an input of 25 watts to the final stage. This power shall be derived from a self-contained and fully portable source. A Portable/Mobile Station shall not be located within one mile radius from the home(s) of the operator(s), nor be situated in any occupied dwelling or building.

Portable/Mobile Stations may be moved from place to place during the Contest.

No apparatus shall be set up on the site earlier than 24 hours prior to the Contest.

All Amateur bands may be used, but no cross-band operating is permitted.

3. Amateurs may enter for either (a) or (b), or both, in the Portable/Mobile sections.

4. One contact per station for phone and one for c.w. per band is permitted.

5. Entrants must operate within the terms of their licences and in particular observe the regulations with regard to portable operation.

6. Serial numbers consisting of RS or RST report plus three figures commencing with 001 and increasing by one for each successive contact shall be exchanged.

7a. Entrants in Section (c) for Multiple Operator Stations can set up separate transmitters to work on different bands at the same time. All such units of a Multiple Operator Station must be located within an area that can be encompassed by a circle not greater than half a mile diameter.

For each transmitter of a Multiple Operator Station a separate log shall be kept with serial numbers starting from 001 and increasing by one for each successive contact. All logs of a Multiple Operator Station shall be submitted by the Operator under whose Call Sign the transmitters are working. No two transmitters of a Multiple Operator Station are permitted to operate on the same band at any time.

7. Scoring:—

(a) Portable/Mobile Stations:

For contacts with Portable/Mobile Stations outside entrant's Call Area 15 points

For contacts with Portable/Mobile Stations within entrant's Call Area 10 points

For contacts with Fixed Stations outside the entrant's Call Area 5 points

For contacts with Fixed Stations within the entrant's Call Area 2 points

(b) Fixed Stations:

For contacts with Portable/Mobile Stations outside entrant's Call Area 15 points

For contacts with Portable/Mobile Stations within entrant's Call Area 10 points

8. The following shall constitute Call Areas: VK1 and VK2 combined, VK3, VK4, VK5 and VK8 combined, VK6, VK7, VK9 and VK0.

9. All logs shall be set out under the following headings: Date/Time (E.A.S.T.), Band, Emission, Call Sign, RST/No. Sent, RST/No. Received, Points Claimed. Contacts must be listed in numerical order.

In addition, there shall be a front sheet showing the following information:—

Name Address
Call Sign Section
Call Sign of other operator(s) (if any)
Location of Portable/Mobile Station
From hours to hours
From hours to hours

A brief description of equipment used, bands used and points claimed, followed by the declaration:

"I hereby certify that I have operated in accordance with the rules and spirit of the Contest."

Signed Date

10. The right is reserved to disqualify any entrant who, during the Contest, has not observed the Regulations and the Rules of this Contest or who has consistently departed from the accepted code of operating ethics.

11. The decision of the Federal Contest Committee of the Wireless Institute of Australia is final and no disputes will be entered into.

12. Certificates will be awarded to the highest scorer in each Call Area. Additional Certificates may be issued at the discretion of the F.C.C.

13. Return of Logs:—

All entries must be postmarked not later than the 8th March, 1964, and addressed to the—

Federal Contest Committee, W.I.A.,
Box 638J, G.P.O.,
Brisbane, Queensland.

RECEIVING SECTION

14. This section is open to all Short Wave Listeners in VK Call Areas. The Rules shall be the same as for the Transmitting Stations. Logs shall take the same form as for Transmitting Stations, but will omit the serial number received.

Logs must show the Call Sign of the Station heard, the serial number sent by it, and the Call Sign of the Station being worked.

Only one lot of points can be claimed for any one contact between two stations, for example: VK2AA/P calling VK3XX/P and exchanging numbers. Points can be claimed only for VK-2AA/P working VK3XX/P. No points can be claimed for VK3XX/P working VK2AA/P during this particular contact.

Scoring will be on the same basis as for Transmitting Stations. It will not be sufficient to log a station calling CQ. A station may be logged once only for phone and once for c.w. in each band.

Awards—Certificates will be awarded for the highest scorer in each Call Area.

S.S.B. CRYSTALS

Set of Five Gold-Plated Matched Crystals


Mounted in HC6U Holders
Suitable for 455 Kc. I.F's.

Price £16-10-0 per Set
+ 12½% Sales Tax

Full details on request.

BRIGHT STAR RADIO

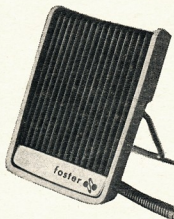46 Eastgate St., Oakleigh,
S.E.12, Vic. Phone 57-6387



DF-2

FOSTER DYNAMIC MICROPHONES FOR HAND-DESK USE

SPECIFICATIONS:

Output Impedance 50 ohms or 50K ohms
Effective output level —55 db. [0 db. = (one) 1V. Microbar]
Frequency response 200 to 10,000 c.p.s.

OMNI-DIRECTIONAL DYNAMIC:

SIZE: 3" x 2-1/8" x 1".
Cable: 5 ft. of P.V.C.
Switch: on-off.
Desk Stand. Clip folds for hand use.
Colour: WHITE.
Plastic Diaphragm.

Retail Price
50K ohms
£2/10/7
+ Sales Tax 5/3

A QUALITY PRODUCT OF EXCELLENT DESIGN



Marketed by **ZEPHYR PRODUCTS PTY. LTD.**
58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA Phones: 25-1300, 25-4556

Manufacturers of Radio and Electrical Equipment and Components

Agents: D. K. Northover & Co.; Neil Muller Ltd.; Homecrafts (Tas.) P/L; Jacoby, Mitchell & Co. P/L; T. H. Martin P/L.

● HERE IT IS! JUST OUT

"CQ's ANTENNA ROUNDUP"

160 pages of sheer enjoyment. Forty-seven information-packed articles. The cream of Antenna information.

Price 35/6, plus 1/6 postage

● FOR THE NEWCOMER!

"UNDERSTANDING AMATEUR RADIO"

A brand new addition to the A.R.R.L. family of publications for the Radio Amateur. The 320 pages of this helpful new publication contains a great amount of "down to earth" information. A "must" for Ham operators.

Price 28/-, plus 1/6 postage

● EVERYBODY'S FAVOURITE!

"THE RADIO AMATEUR'S HANDBOOK"

1963 Edition

The standard manual of Amateur Radio Communication.

Price 51/6, plus 2/6 postage

● THIS IS GOOD!

"AMATEUR RADIO ANTENNA HANDBOOK"

by HARRY HOOTEN

A complete coverage of Ham Antenna Systems including theory and practical design application, transmission lines, impedance matching, coupling, "home-brew" arrays, and towers. Send your order now.

Price 31/3, plus 1/9 postage

MCGILL'S AUTHORISED NEWSAGENCY

Established 1860.

183-185 ELIZABETH STREET, MELBOURNE, C.1, VIC.

"The Post Office is opposite"

Phones: 60-1475-6-7

Recent Trends in Receiver Front-End Design*

Noise Figure and Cross Modulation Characteristics of Tube and Transistor Front Ends

E. A. ANDRADE, WODAN

EARLIER "QST" articles,^{1,2,3} have painted a fairly comprehensive picture of the performance to expect of a modern high-quality communications receiver. Superhetrodyne front-end performance has certainly come a long way from the days of the National FB-7 (a very advanced receiver for its day, indeed!), with its two metre bands 910 Kc. apart, to the modern double-conversion crystal controlled s.s.b. receiver.

Two recent trends in receiver design, the band-passed front end and the transistor front end, will be discussed in this article. Means of minimising some of the problems will also be discussed.

Before proceeding, it might be well to review the requirements for a good communications receiver r.f. section.

SENSITIVITY

The receiver must have enough amplification to make the weakest signals audible in the loudspeaker. Such amplification is fairly easy to attain in the modern superhetrodyne, where gain may be obtained at several different frequencies. The gain can be relatively low at any one of the frequencies, so gain stability is not a serious problem. The gain from antenna to loudspeaker in a typical communications receiver may be as high as 10 million.

However, all this gain will not allow the operator to copy a weak DX signal unless the signal-to-noise ratio is adequate. This means that the noise contributed by antenna coupling circuits, r.f. amplifiers and mixers must be held to a minimum.

The best way to express receiver sensitivity is either in terms of signal-to-noise ratio—or even better—in terms of noise figure.

It is generally agreed that in the h.f. spectrum (2 to 30 Mc.) a noise figure of 6 to 7 db. is all the sensitivity that can be used because of the masking effects of antenna noise, provided that a matched antenna system is used. In our discussion we will consider this sensitivity adequate. For a further discussion of noise figure, see references 1 and 2.

CROSS-MODULATION

Unfortunately, adequate gain and sensitivity are not the entire story in a communications receiver. An often neglected area of front-end design is its performance in the presence of strong signals out of the pass-band.

If we are listening to a weak DX signal with an S meter reading of, say,

● Building a receiver for immunity to cross-modulation calls for compromising on other desirable features. Here is a discussion of receiver front-end design that the man who makes his own can't afford to miss.

S2 and a strong local comes on the air, perhaps 50 Kc. removed from our DX station's frequency, the modulation of the undesired signal may appear on the weaker signal. This effect is known as cross-modulation. In the case of single-sideband signals, the splatter that you have been blaming on the other fellow's signal could be generated in your own receiver by its cross-modulation.

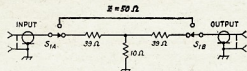


Fig. 1.—Circuit of 20 db. "T" pad for insertion in coaxial line. Values given are for 50-ohm line. Resistors are ½ watt composition. S1 is a d.p.d.t. toggle switch. Coax connectors may be any type.

Another effect, closely related to cross-modulation, is desensitization, or blocking. This occurs when a strong off-channel signal actually drives the r.f. amplifier or a mixer into grid current so the tube biases itself toward cutoff. Generally, if the cross-modulation capabilities of a receiver are adequate there is no trouble from blocking effects.

Cross-modulation performance of a receiver is usually plotted for a fixed level of desired signal in the passband against various levels of undesired signal that cause cross-modulation 10 db. below the desired signal audio level.

If you suspect that your receiver is cross-modulating, an easy check may be made by inserting a 20-db. pad between the receiver and the antenna. The desired signal is usually strong enough so that it may still be heard. However, if the interfering signal is the result of receiver cross-modulation, it will disappear when the pad is inserted. Fig. 1 gives the circuit and values for a 20-db. pad. The pad should be shielded to prevent stray pickup, and the construction should be such as to minimise capacitive coupling between the input and output connectors.

THE BAND-PASSED FRONT END

A considerable simplification in the tuning mechanism of a multiple conversion receiver may be accomplished by replacing all signal-frequency tuned i.f. circuits with suitable broad-band transformers, usually designed just to accommodate one Ham band. The

receiver band switch then selects the proper transformer for the desired band. The reduction in mechanical complexity is certainly very attractive, particularly to the home constructor. Unfortunately, a serious penalty in cross-modulation performance, and to a degree sensitivity, is incurred.

Cure D in Fig. 2 shows the cross-modulation of a typical commercial receiver having a broad-band front end, compared to one (Collins 75A-4) which uses two tuned circuits at r.f., Curve B. The curves were taken with a 5 μ V. desired signal, both the desired and undesired signals being fed to the 50 ohm receiver input. For undesired signal levels of 0.1 to 1.0 volt, the cross-modulation occurs essentially in the r.f. amplifier tube of a tuned receiver. In a broad-banded receiver it usually occurs in the first or second

mixer. Cross-modulation of undesired signal levels below 0.1 volt generally occurs in the mixer stages, in a tuned receiver, unless extremely low r.f. amplifier gain and very high antenna-coil gain are used. The noise figure of the broad-band receiver was considerably poorer than the 75A-4, as a result of a compromise in antenna-coil gain in order to minimise cross-modulation as much as possible.

The poorer performance of band-pass circuits would be most noticeable on the three lower-frequency bands, 3.5, 7 and 14 Mc. As the signal frequency is increased, the effective selectivity of

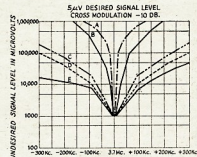


Fig. 2.—Cross-modulation characteristics of various types of receiver front end. The curves show the undesired-signal input, as a function of frequency, required to produce cross-modulation 10 db. below the output from a 5 microvolt desired signal on 3.7 Mc.
A—Tuned r.f. amplifier using a 6306 tube.
B—Collins 75A-4.
C—Broad-band r.f. amplifier using 6306.
D—Commercial broad-band receiver.
E—Transistor front end.

* Reprinted from "QST," June, 1952.

1. Goodman, "How Sensitive Is Your Receiver?" "QST," September, 1947.

2. Papenfuss, "A Discussion of Receiver Performance," "QST," January, 1952.

3. Papenfuss and Andrade, "Modifying 75A-3 and 75A-3 Receivers," "QST," July, 1953.

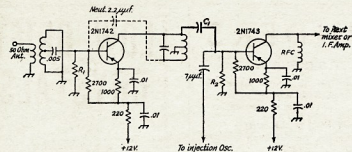


Fig. 5.—Transistor r.f. amplifier and mixer circuit. Capacitances are in μF , except as indicated; resistances are in ohms; resistors are $\frac{1}{2}$ watt. See text for adjustment of antenna coil tap. Interstage coil centre-tapped.

Cl—Selected for desired r.f. stage gain; typically 7 pF.

R1—Approximately 12,000 ohms; adjust for 3.5 mA. collector current.

R2—Approximately 18,000 ohms; adjust for 1.0 mA. collector current.

proper value for R1 (approximately
12,000 ohms)

Fig. 6 is a plot of input capacitance and input impedance vs. frequency, for various values of collector current, for the 2N1742. If the 2N1742 is used in the 3-30 Mc. frequency range, neutralisation will probably not be necessary. However, if it is used at higher frequencies than 30 Mc., it would be desirable to add the network shown dotted in Fig. 5, to realise the maximum power gain and minimum noise figure.

CROSS-MODULATION IN TRANSISTOR R.F. STAGES

As stated previously, cross-modulation is a serious problem in transistorised receivers. R.f. transistors have an inherently limited dynamic range and will cross-modulate with some 20 to

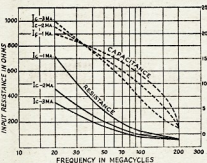


Fig. 8.—Typical equivalent parallel input resistance and capacitance, 2N1742 with V_{ce} equals —10 volts, for selected values of collector current, output short-circuited.

30 db. less signal than a tube stage. Although to date no one has come up with a good answer to the problem, there are a few design tricks that help to minimise it.

The most simple device to minimise cross-modulation would be a 20-db. attenuator with a switch to connect it between the antenna and the receiver input stage when a strong off-channel signal is cross-modulating. Perhaps this sounds a bit agricultural, but it works, provided the desired signal is strong enough to overcome the 20-db. loss. Admittedly, this ruins the noise figure of the receiver, but there's not much point in having a 6 or 7 db. noise figure

when a strong local is wiping out the whole band.

A more exotic way of improving the r.f.-stage cross-modulation would be to improve the r.f. selectivity by using two or even three tuned circuits ahead of the r.f. transistor. Noise figure would suffer to a degree, but this is a compromise that the receiver designer is frequently required to make, even in a tube receiver.

Another means of improving the cross-modulation is to introduce degeneration in the emitter lead of a common-emitter r.f. stage. Caution must be exercised to assure that no more than 3 or 4 db. of degeneration is used, or the noise figure will deteriorate excessively. Other negative feedback schemes have been considered, but stability becomes a problem if any great amount of r.f. feedback is used.

TRANSISTOR MIXERS

A transistor used as a mixer will generally provide about 3 db less gain than the same transistor operated as an r.f. amplifier. This is considerably different from tubes, where the conversion gain is approximately 25 per cent. of the tube's gain as an amplifier. R.f. gain in transistor front ends must be held to the minimum consistent with the desired noise figure, just as in a tube r.f. section; otherwise, mixer cross-modulation will become excessive.

A 10 to 12 db. mixer noise figure is fairly common for transistor mixers such as Philco 2N1743. In order to realise this noise figure, careful attention must be paid the recommended collector current and oscillator injection power requirements for the

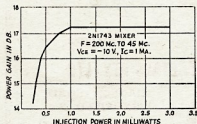


Fig. 7.—Gain vs. oscillator injection power, 2N1743 as a mixer with Vce equals -10 volts, Ic equals 1 mA. This curve applies over the frequency range 45-200 Mc.

particular transistor being used. Fig. 7 shows the effect of collector current on noise figure, and Fig. 8 shows oscillator injection power vs. mixer gain.

The formula for computing the effect of mixer noise figure on r.f. stage noise figure is

$$\text{Noise figure (power ratio) } F_{ab} = \frac{F_a + \frac{F_b - 1}{A}}$$

where F_{ab} is the total noise figure, F_a is the noise figure of the r.f. amplifier, and F_b is the noise figure of the mixer. These are expressed as power ratios. To get the noise figure in db., take 10 times the log₁₀ of the power ratio. A is the power-gain ratio of the r.f. stage including all coupling losses between stages. A numerical example is given below:

$$F_a = 4 \text{ db.}; \text{ power ratio} = 2.5$$

Fb = 10 db.; power ratio = 10

$A = 10$ db.; power ratio = 10

Therefore, $F_{ab} = 2.5 + \frac{10 - 1}{10}$

$$= 2.5 + \frac{9}{10} = 3.4$$

$$10 \times \log_{36} \text{ of } 3.4 = 5.3$$

$$F_{ab} = 5.3 \text{ db.}$$

The noise figure (5.3 db.) is now referenced from the base of the r.f. amplifier transistor. Antenna-coupling circuit losses must also be considered in determining the over-all noise figure of the receiver. Although it is possible


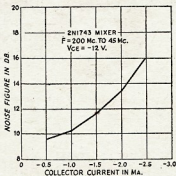


Fig. 8.—Noise figure vs. collector current, 2N1743 as a mixer, 45 to 200 Mc.

to compute the over-all noise figure including the antenna-coil tuned-circuit losses, it becomes somewhat involved because three variables affect it. These are the losses inherent in the tuned circuit (Q), losses due to mismatching, and the effect on transistor noise figure with change in source impedance. The computation of this is somewhat beyond the scope of this article. However, a good approximation may be made by setting the transistor tap on the input coil to match the input impedance of the transistor, measuring noise figure, and then moving the tap as close to the ground end of the coil as you can get while still maintaining a 7 db. noise figure. This will keep signal levels to the r.f. stages as low as possible, thereby minimising cross-modulation.

Needless to say, it is very desirable to use as high a tuned-circuit coil Q

(Continued on Page 21)

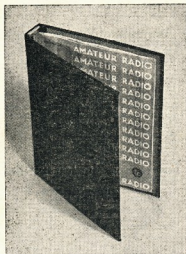

BINDERS

for "Amateur Radio"

- ★ Solid Cover bound in black Fabrex with wire attachment for easy filing of copies.

Price 19/6 each

Postage extra. Vic. 2/-, Interstate 3/-


Polar Diagram Graph Paper
for Radiation Patterns

Price 1/- sheet. Size: 12" diameter.
42/6 pad of 50 sheets.

NORMAN BROS. PTY. LTD.

60 ELIZABETH STREET,
MELBOURNE, C.1, VIC.

CHOOSE THE BEST—IT COSTS NO MORE

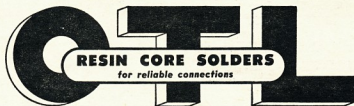

O. T. LEMPRIERE & CO. LIMITED. Head Office: 27-41 Bowden Street, Alexandria, N.S.W.
and at Melbourne • Brisbane • Adelaide • Perth

DURALUMIN, ALUMINIUM ALLOY TUBING

IDEAL FOR BEAM AERIALS AND T.V.

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS— $\frac{1}{4}$ " TO 3"

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

GUNNERSSEN ALLEN METALS PTY. LTD.

SALMON STREET,
PORT MELBOURNE, VIC.

Phone: 64-3351 (10 lines)
Telegrams: "Metals," Melb.



HANSON ROAD,
WINGFIELD, S.A.

Phone: 45-6021 (4 lines)
Telegrams: "Metals," Adel.

LOW DRIFT CRYSTALS

FOR

**AMATEUR
BANDS**

ACCURACY 0.02% OF
STATED FREQUENCY

3.5 and 7 Mc.

Unmounted, £2/10/0

Mounted, £3/0/0

12.5 and 14 Mc.
Fundamental Crystals,
"Low Drift,"

Mounted only, £5.

THESE PRICES DO NOT
INCLUDE SALES TAX.

Spot Frequency Crystals
Prices on Application.

Regrinds £1/10/0

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY, E.7,
VICTORIA

W.I.A. N.S.W. DIVISION
15th Annual Convention

A FIELD DAY

will be held at

V K 2 W I

Quarry Road, Dural

on

SUNDAY, 26th JAN., 1964

Transmitter Hunts, Mobile Efficiency
Test, Disposals, Competitions, QSL Bur-
eau and Demonstrations.

Registration 10/-
XYL and Harmonics Free

FREQUENCY MARKER WITH 50 Kc. INTERVALS

SOME of the luckier Amateurs have equipment with 100 Kc. calibrators built in and for them band-edge spotting is no problem, except where again is 7150, 14350 or 21450 kc.?

In looking up some information recently on frequency sub-dividers, multi-vibrators, I struck an old "QST" article describing a crystal oscillator locked 50 kc. multi-vibrator, and one evening decided to put it together in a hurry and see how it worked. Well, it works beautifully with a 400 or 500 kc. crystal, which are not so elusive as the 100 kc. rocks, nor so expensive, and because of the square wave output nature of the multi-vibrator, there is plenty of signal down to 10 metres!

Only two tubes are required, a pentode as Pierce crystal oscillator with provisions to adjust the crystal frequency up or down a bit and zero beat it against a frequency standard, and a triode-pentode with a 50K potentiometer to adjust the multi-vibrator frequency and make it lock in with the correct crystal submultiple (don't know a better word!).

Power consumption is very small, so could be taken from the existing receiver. Because of the simplicity of the circuit, no construction details or pictures are given. 400 or 500 kc. crystals can be procured from advertisers in "A.R."

—Arie Bles, VK2AVA.

RECEIVER FRONT-END DESIGN

(Continued from Page 19)

as possible in order to maintain the maximum r.f. selectivity for best cross-modulation performance.

AUTOMATIC GAIN CONTROL

The choice of an a.g.c. system in transistorised r.f. sections may have a considerable effect on cross-modulation characteristics of the receiver. In general, "forward" a.g.c., which reduces transistor stage gain by lowering the emitter to collector voltage, will provide better cross-modulation performance than the conventional "reverse" a.g.c., which controls gain by varying the base bias to reduce collector current in a manner similar to the bias control used with remote-cut-off pentodes.

Even better results can be obtained with a.g.c. systems where the controlled element is separate from the transistor stage. An example of this would be some form of a bridge or "T" network using a voltage variable capacitor, controlled by a.g.c. voltage.

CONCLUSION

As our technology expands, new tools for accomplishing our radio communication jobs are evolved. They are not always a direct advance in the state of the art, but must be considered carefully in the light of existing requirements.

In the case of the broad-band circuits discussed in this article, we have a definite step backward in cross-modulation and blocking capability. Modifying circumstances such as the need for light weight, portability, low power drain, low cost, or mechanical simplification may be worth the sacrifice in performance that accompanies the use of these design techniques. ●

GEOLO TRANSMITTER

(Continued from Page 3)


prodding and wriggling the net switch can be dismantled and the extra wafer installed without removing any wires.

This new wafer is wired in such a way that the bleed resistor circuit is made in the a.m. and c.w. positions, but is opened on net.

The mounting of the relay is a matter of individual choice, but I found that by bending the vertical shield between the v.f.o. and final amplifier sections over at an angle of 45°, a small shelf was made on which the relay could be mounted in a position where all wires would reach without being cut or extended. Power for the relay will, of course, depend on the type. Mine is an industrial type with 230v. coil which is triggered by an extremely small single pole relay with a very high resistance coil operated from the in-built bias supply.

At first sight it may appear necessary to replace the 33 ohm resistor with a heavier one, but mine has been operating for nearly a year now without ill effect.

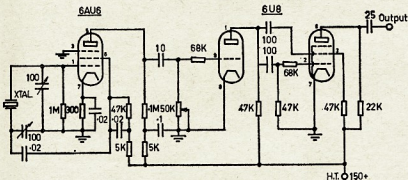There is nothing very complex about these modifications. They do, however, make what is already a very efficient transmitter even more convenient to operate. ●



BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY AND OUTPUT

Our Crystals cover all types and frequencies in common use and include overtone, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, B7G, Octal, HC-18U.

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE AVAILABLE IN FT243 HOLDERS:—

6280, 4095, 4535, 2760, 2524 Kc.

5500 Kc. T.V. Sweep Generator Crystals, £3/12/6.

100 Kc. and 1000 Kc. Frequency Standard, £8/10/0 plus 12½% Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on application.

455 Kc. Filter Crystals, vacuum mounted, £6/10/0 each plus 12½% Sales Tax.

ALSO AMATEUR TYPE CRYSTALS—3.5 AND 7 Mc. BAND.

Commercial—0.02% £3/12/6, 0.01% £3/15/6, plus 12½% Sales Tax.

Amateur—from £3 each, plus 12½% Sales Tax.

Regrinds £1/10/-.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carrel, Box 2102, Auckland. Contractors to Federal and State Government Departments.

BRIGHT STAR RADIO

46 Eastgate Street, Oakleigh, S.E.12, Vic.

Phone: 57-6387

With the co-operation of our overseas associates our crystal manufacturing methods are the latest.



ADDRESS CORRESPONDENCE FOR THIS PAGE DIRECT TO THE SUB EDITOR

Amateur Radio, January, 1964

HE S W L

TYPE F1 EMISSION

Postmaster-General's Department

Treasury Place,
Melbourne, C.2, Vic.
13th Nov., 1963

Federal Secretary,
Wireless Institute of Aust.,
Box 2611W, Melbourne.

Dear Sir,

Further to our letter dated 26th July, 1963, in connection with type F1 emission in the Amateur Service (your letter of the 8th September refers), arrangements have now been made with effect forthwith to include type F1 emission, employing a maximum frequency shift of 850 c.p.s., in the type of emission permitted for use by the Amateur Service within all authorised frequency bands. The use of type F1 emission shall be confined to radio-teletype (R.T.T.Y.) systems employing a teleprinter type equipment using perforated tape or direct keyboard transmission and a printing mechanism for reception. The use of hand-speed Morse utilising type F1 emission is prohibited. R.T.T.Y. transmissions shall employ a five-figure N code in accordance with International Alphabet No. 2.

For purposes of station identification in accordance with paragraphs 132 and 133 of the "Handbook for Operators of Radio Stations in the Amateur Service," July, 1963, which read—

"132. The operator of an Amateur Station shall transmit the call sign of the station being worked and the call sign allotted to the station that he is operating at the beginning and end of each session, and at least once in every five minutes during the session.

133. Call signs must, in all cases, be signalled in full and in such a manner as to leave no doubt as to their identity, and must include the nationally prefix letters 'VK'."

an Amateur Station licensee employing type F1 emission shall transmit call signs either by means of hand-speed Morse (type A1) or radio telephony (types A3 or F3) signals.

It is not proposed that the Department inform each Amateur Station licensee of the new condition at this stage, but it would be appreciated if you would be good enough to arrange for appropriate publicity through the Institute's Divisional Broadcasts and Magazine "Amateur Radio," please.

Yours faithfully,

(Sgd.) L. F. Pearson,
for Director-General.

NEW SOUTH WALES

During 1963 the VK3 Group showed a marked improvement on previous years. Attendances at the meetings were quite good. I feel sure that if more of our Group would come along they would enjoy what is offered and would certainly come again. Our thanks go to Phil Z2PI and Tim Z2TM for their continued support, and their patience in imparting knowledge which is a great inspiration to a.w.l.s. We are indeed fortunate in having two such stalwarts who are always there to help us on our way.

Our October meeting was a great success. Phil Z2PI gave an interesting talk on how to construct an all-band antenna and explained a three-transistor converter for 3.5, 7 and 14 Mc. If any a.w.l. would like a copy of the above converter circuit, just drop me a line, plus a stamp and my yours.

Our Secretary still has a few copies of the ARF manual on hand and members can purchase same for 10/6 plus postage. Write to Fom Harding, 33 Waratah St., Berowra, N.S.W.

We offer our congratulations to Ross L2233/VK4 and to L2623 for their respective wins in the last N.P.D. Contest, good work lads.

Sid L2258 has his AMR300 going on all bands except 80 m. at the moment. He sends word of logging OA, Gx and F2, which is not bad going on any rx. Sid intends having a go for his ticket and we wish him well.

Ross L2233/VK4, who lives in the Rockhampton area, sends news of the prospects of a new rx, a GR59. He intends to use his 16RT for portable work and the other for his fixed station receiver.

Chas. L2211 reports that his 50 Mc. converter is not working, but Vince VK3VC has the matter under control.

Thought for the month: Use the right tool for the right job. 73, Chas. L2211.

DX LADDER

	Countries		Zns.	S.s.b.	W
	Conf.	Hrd.	Conf.	Hrd.	St.
E. Trebilcock	282	289	40	—	50
D. Grantley	113	272	38	20	104 35
A. Westcott	93	159	31	9	107 11
M. Hilliard	83	235	33	29	165 12
M. Cox	80	229	29	29	150 18
P. Drew	66	199	27	29	131 14
C. Abernethy	56	96	30	—	—
N. Harrison	44	119	29	4	20 35
I. Thomas	42	139	20	16	97 14
G. Earl	38	131	22	30	104 3

Wireless Institute of Australia

Victorian Division

A.O.C.P. CLASS

commences

MONDAY, 10th FEB., 1964

Theory is held on Monday evenings, and Morse and Regulations on Thursday evenings from 8 to 10 p.m.

Persons desirous of being enrolled should communicate with—

Secretary W.I.A., Victorian Division, P.O. Box 36, East Melbourne (Phone: 41-3535, 10 a.m. to 3 p.m.), or the Class Manager on either of the above evenings.

The DX has arrived on 6 metres and each State is working its share. Many new calls are appearing and some old ones are being used again. All States VK1, 2, 3, 4, 5, 6, 7, 8, 9) are represented, so with just a fair share of luck and good conditions there should be an increase in the 50 Mc. W.A.S. certificate award.

VK3ZBV has been down south into VK3 on 29th Nov. A signal on 50.75 which could be Z2CX has been heard on occasions in VK3 but no identification on the carrier.

JAs have been heard on at least three days during November in VK3. VK3ZBN scored JAZAYM on 24th. I was copying the JA but could not positively identify him at the same Ron worked him at 1400. Others heard JAs as early as 0630 same day.

Northern VK4s have also been amongst the JAs in recent weeks.

The band has been open from ZL to VK since 23rd. First in VK3 on 27th with ZL3 and almost daily until end of the month.

Numerous odd signals from VK5 and VK7 heard in VK3 during openings, but nothing worked to date. Nothing heard from VK6 since end of November.

The early closure of the notes leaves the page a little bare for this month. 73, ZSGP.

QUEENSLAND

The v.h.f. meeting was held on Friday, 15th Nov., with about a dozen members present. At the meeting was the latest arrival on six metres—Roy Z4ZF, who puts out a fine signal from Annerley. Also on the air is Ron Z4RJ who has recently returned from VK3. His operating frequency is 42.45 Mc. and using 13w. to a 5763 and quarter wave length of hook-up wire. By the time you read this, he will have a 2 element beam in operation.

At the time of writing these notes, Malcolm Z4ZEL and Allan Z4ZAW are mobile somewhere in VK3. George Z4ZLG is mobile and will be going to VK3 at the end of November.

The summer DX is coming good with VKs 1, 2, 3, 5 and 7 being worked and a VK6 has been heard also.

Victor Z4ZBT gave a lecture on Satellites to the monthly meeting of W.I.A. Several of the Brisbane boys are interested and will endeavour to track the satellite. 73, Z4ZDF.

WESTERN AUSTRALIA

Here in W.A. the coming of the summer months has meant a considerable rise in v.h.f. activity and as well as hearing a number of seldom-heard call signs on the air, a number of W.I.A. Group projects are also under way.

The 50 Mc. beacon tx which has been in operation at Cocos Is. for some time is being returned to Perth for an overhaul and it is planned to send it to Christmas Island where it will be operated by members of the Christmas Island Radio Club.

By the time that these notes are in print the new VK6VF beacon should be on the air and the details of operation are: Freq., 50.002 or 50.002 Mc. (depending on when the 50-53 Mc. band last operation, virtually 24 hours a day; identification, call sign VK6VF keyed by using frequency shift keying (850 c.p.s. deviation); power, about 40 watts.

It is unfortunate that the new beacon was not ready for use sooner, but a considerable amount of work is entailed in building a beacon which is to run continuously. The 50 Mc. beacon is incidentally ran for a total of about 20,000 hours, using the original output valve (an 807).

A number of 70 Mc. f.m. mobile transceivers have been purchased by the Institute in conjunction with the W.I.C.E.N. organisation in this State and these units are being modified for use on the 50 Mc. band. Small quantities of 70 Mc. a.m. mobile transceivers are also starting to become available, but it hasn't been decided how these will be used yet. There is a chance that these units could be converted to f.m. operation with surprisingly little work and if this is the case they will be used to expand the 50 Mc. f.m. net.

The only other news of interstate interest is that Trevor G2DZ will be operating portable in Adelaide during the University vacation and no doubt those in VK3-kind will know that he is around by this time. 73, G2DZ.

Preliminary details of the 1964 A.R.R.L. International DX Contest have been received. The dates are: Phone, Feb. 8/9 and March 14/15; C.w., Feb. 22/23 and March 28/29. The rules are unchanged from 1963.

—Ray Jones, VK3RJ, Manager.

The December meeting of the Branch took the form of a combined Christmas meeting and welcome back to Llonel 2CS. A large gathering of 45 members, visitors and associates, including quite a number of ladies, watched with great interest as the guest of honour, Llonel, showed and commented on a number of very interesting projected transparencies illustrating his world tour. All this, together with the pleasant chat after the meeting, made for a most enjoyable evening and all who attended agreed.

Federal Executive, on behalf of the Federal Council of the Wireless Institute of Australia, hereby gives notice that it is intended to alter the Federal Constitution of the Wireless Institute of Australia 1947 as follows:—

"21. The Headquarters Division shall call for nominations annually from its members for appointment to the Federal Executive, such nominations to be received not less than 60 days prior to the conclusion of the fiscal year. The nominations which shall include the names of any retiring members of the Division shall be willing to re-nominate shall be submitted by the Headquarters Division to Federal Council for the appointment by preferential vote of seven members, two at least of whom shall be retiring members."

"21a. The new Federal Executive shall take office at the conclusion of the Federal Convention which they shall attend, or where a Federal Convention is not held, within one month of the conclusion of the fiscal year. The Federal Executive shall determine its own offices in such manner as considered necessary."

"24. The appointment of Federal Executive which shall be finalised by the Headquarters Division not less than 14 days prior to the conclusion of the fiscal year shall be notified in writing to Federal Council prior to the conclusion of the fiscal year. The Federal Executive shall notify the Federal Council of the names of the officers and appointees thereof within 28 days of the commencement of the new fiscal year or the Federal Convention whichever is the sooner."

Any member of the Institute not in agreement with the proposed alterations should notify his disapproval and the reasons to the Federal Secretary within 14 days of the publication of this proposal.

The new address for the W2-K2 QSL Bureau is North Jersey DX Association, P.O. Box 303, Bradley Beach, N.J., U.S.A.

Graham VK2AGH will handle any cards for VK4HG and VK4WV who were at Willis Island and also for VK4JQ who is presently at Willis.

Albert Zander, VK3PG, who was active on the h.f., v.h.f. and u.h.f. bands for many years until 1960, has decided to make a comeback. Bert has acquired some very fine gear and should soon be heard on s.s.b. and later on c.w. Gear consists of HT transmitter, SX receiver and a TA33 Jnr. mounted on a fine tower.

Bruno Boert, HB9QO, was due to arrive in Australia on 28th November and after a stay of about six weeks in Sydney will come on to Melbourne where he will be employed by Landis and Gyr for about two years. Bruno hopes to become active under a VK call sign. Writer had the good fortune to meet Bruno at his home at Nottwil just outside Lucerne.

**Repairs to Receivers, Transmitters;
Construction and Testing; T.V. Align-
ment; Low Noise Xtal Conv., any fre-
quency. £18/10/0 plus tax.**

ECCLESTON ELECTRONICS
146a Cotham Road, Kew, Vic. WY 3777.

Around 26/11/63 2AXR visited southern VK7 and was shown around quite a few of the shacks. Al was relieving Radio Officer aboard the Patina on the Sydney-Hobart run. Hope you enjoyed your brief visit Al and will be back again some time. Ian ZZZ is back on deck again and once again hard at work. Still finds time for the DX though, and recently worked VKOBE (VK7ZBE) down in the white wastes. Brian is apparently having a whale of a time at a party. Hot days—up around 27 degrees. Knowing Brian, I guess he's around the life of the party down there.

During the latter part of October, Snowy TCH operated maritime mobile from his yacht in the vicinity of Brunel Island for a week. The Hamfest at Cambell Town in November was a success with an attendance of 47 members. A good time was had by all and the weather was reasonably good for camping, just holding off a really strong blow towards the end of Sunday afternoon. Look forward to seeing you there again next year. An article will be published in the mag, later this year giving details of the weekend's activities.

That's it for this month camp, all the best for the New Year, 73, Mike TCH.

Minimum 5/-, for thirty words.

Extra words, 2d. each.

Advertisements under this heading will only be accepted from Institute Members who desire to dispose of equipment which is their own personal property. Copy must be received at P.O. Box 36, East Melbourne, C.E. Vic., by 8th of the month, and remittance should accompany the advertisement. Call signs are now permitted in Hamads. Dealers' advertisements not accepted in this column.

FOR SALE: Collins ART13 Transmitter, 813 final modulated by two 811s, good disposals condition, unmodified, complete with low frequency v.f.o., original supply, large manual, and all tubes, £25. ATR2B Transceiver, working with all tubes and d.c. power supply £15. 1 only 122, complete with power supply, etc., unmodified, good working condition, £15. 1 only 122, complete with power supply, valves, etc., but not working, £5. VK2AAK, Kulnura, N.S.W.

FOR SALE: Prop. Pitch Motor £10.
6 Kc. a.m. Mechanical Filter, brand
new and unused, £7/12/6. H. Hep-
burn, VK3AFQ, 4 Elizabeth St., East
Brighton. Vic. 96-2414 evenings.

As these notes appear the old year will be gone and the new one off to a bright start, as the conditions appear to be on the up grade. European stations can be heard coming through in the afternoon and everyone of us trying to get a contact with the reluctant bedlam.

The near north causing some consternation due (maybe) to the conditions interfering with the outback radios on the Flying Doctor Service and the Ambulance Service. Looks like the I.T.U. band allocations are being disregarded. Wonder what would happen if it

Things are very quiet here locally and not many working the 14 Mc. band, although can hear a few of the old timers rag-chewing on 7 Mc. and seem content to let the DX stations go by. Apparently they have given up the rat race in chasing those elusive awards, which seems to get many in

FOR SALE: 1 only 12 volt Tafaz (imported) Transistorised Power Supply for Swan or Collins, or similar, Transceiver. Good condition, very little use and very compact. £60. VK2AAK, Kulnura, N.S.W.

SELL your own **Personal** gear through Hamads. Persons trading in any line, regardless of price, or quantities of similar articles, will be charged commercial rates.

WANTED: Xmitter, all bands, c.w.-a.m. or c.w.-s.s.b., 100 watts max. Also all-band 3 element beam. Bill Barber, VK6DX, 15 Whitlock Street, Kelgoorlie, W.A.

WORLD RANGE RECEIVERS — TRANSMITTERS — TRANSCEIVERS



HALLICRAFTERS:

SR150 TRANSCEIVER
SR160 TRANSCEIVER
HT32B TRANSCEIVER
HT44 TRANSMITTER
HT45 LINEAR AMPLIFIER
SX117 AMATEUR RECEIV'R
SX122 GEN. COV. RECEIVER
SX110 GEN. COV. RECEIVER
SX118 GEN. COV. RECEIVER
S108 GEN. COV. RECEIVER
S120 GEN. COV. RECEIVER
SX115 AMATEUR RECEIV'R
XMITTER ACCESSORIES


SWAN (Right):

SW240 VK TRIBAND
TRANSCEIVER
SW240 AC POW. SUPPLY
SW12 DC POW. SUPPLY
SW-VFO/TCU TRANS-
CEIVER, VFO, VOX,
SPK, CAL, and POWER
SUPPLY.



DRAKE (Below):

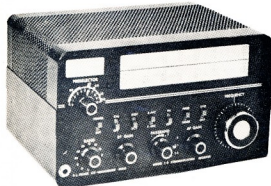2B AMATEUR RECEIVER
TR3 TRANSCEIVER
ACCESSORIES by B. & W.
W.R.L., HYGAIN, and
BANDSPANNER.



THESE ARE A SELECTION OF THE WORLD'S FINEST

Short Wave Equipment is available from:—

N.S.W.: ATLANTIC RADIO

36 Oxford Street, Woollahra — — — Phone 31-7811

W.F.S. ELECTRONIC SUPPLIES CO.

225 Victoria Road, Rydalmere — — — Phone 638-1715

VIC.: ELECTRONIC SERVICES PTY. LTD.

10b Douglas Street, Noble Park — — — Phone 746-8446

S.A.: TELEVISION & RADIOTRONICS

12a Gays Arcade, Adelaide — — — — — Phone 23-2474


QLD.: GENERAL IMPORT DISTRIBUTORS

135 Lutzow St., Wellers Hill, Brisbane — Phone 48-5096

W.A.: NEIL JAMES & CO.

Barrack Street, Perth — — — — — Phone 24-8961

science in electronics...

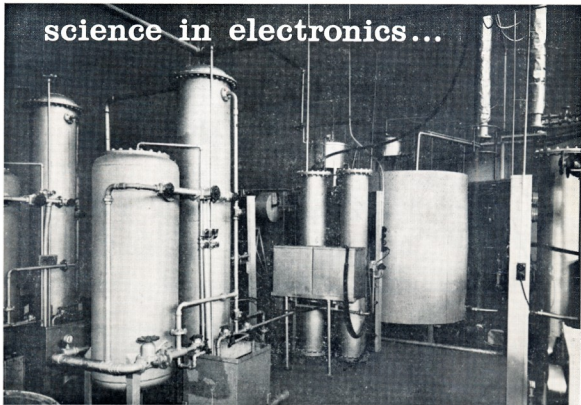

AWV CONTINUOUS-TREATMENT WATER PURIFICATION PLANT

WATER PURIFICATION

Since tap-water contains sedimentary, organic and inorganic impurities it needs intensive purification before it can be used in an electronics factory, for example, for picture tube screen settling or in transistor manufacture.

A continuous-treatment water purification plant has been developed at A.W.V. in which initially chlorine is used to destroy slime-forming organisms and sediments are removed by coagulation and settling. The treated water is then passed through sand filters to remove suspended particles and through activated carbon filters to remove free chlorine. Inorganic salts are then eliminated by means of mixed-bed ion-exchange equipment.

The degree of purification obtained in the A.W.V. plant is such that the greatest metallic impurity is less than one part in ten million, total solids are less than one part in a million and the water is virtually an insulator—the resistance between opposite faces of a one centimetre cube is from five to ten megohms!



AMALGAMATED WIRELESS VALVE CO. PTY. LTD. • SYDNEY • MELBOURNE • ADELAIDE • BRISBANE